

The Path to Efficient-yet-Linear Watt-class mmWave CMOS PAs: Device Stacking, Switch-mode Operation, Power Combining and Linearization

Ritesh Bhat, Anandaroop Chakrabarti and
Harish Krishnaswamy





 **COLUMBIA UNIVERSITY**
IN THE CITY OF NEW YORK

Outline



- Motivation
- Stacking and Switch-mode Operation
- Large-scale Power Combining
- Linearized High Backoff-Efficiency Power DAC employing
Supply Switching and Dynamic Load Modulation
- Conclusion

Motivation

 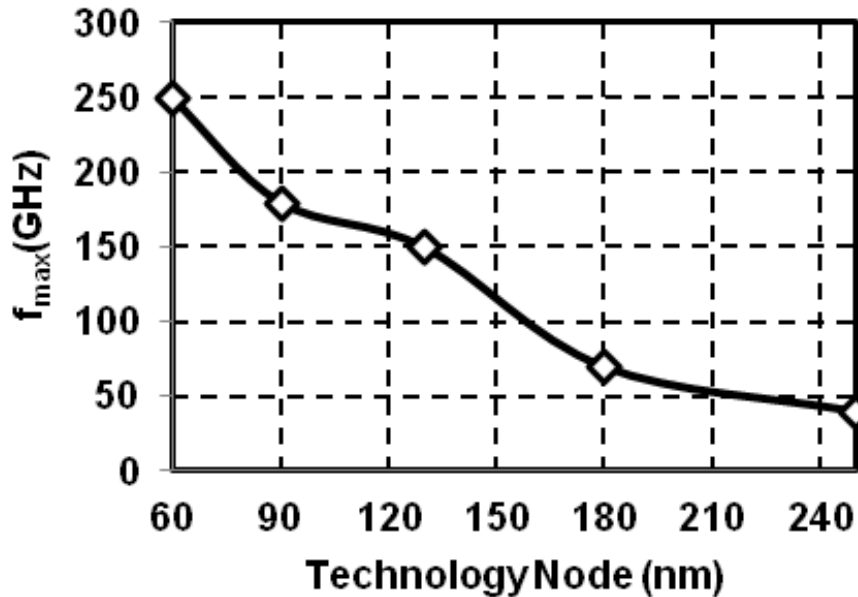

- Operation at mmWave frequencies requires scaled technologies with low breakdown voltages, limiting the output power that can be generated from a single PA.
- Efficiency is limited by active and passive losses.

Motivation

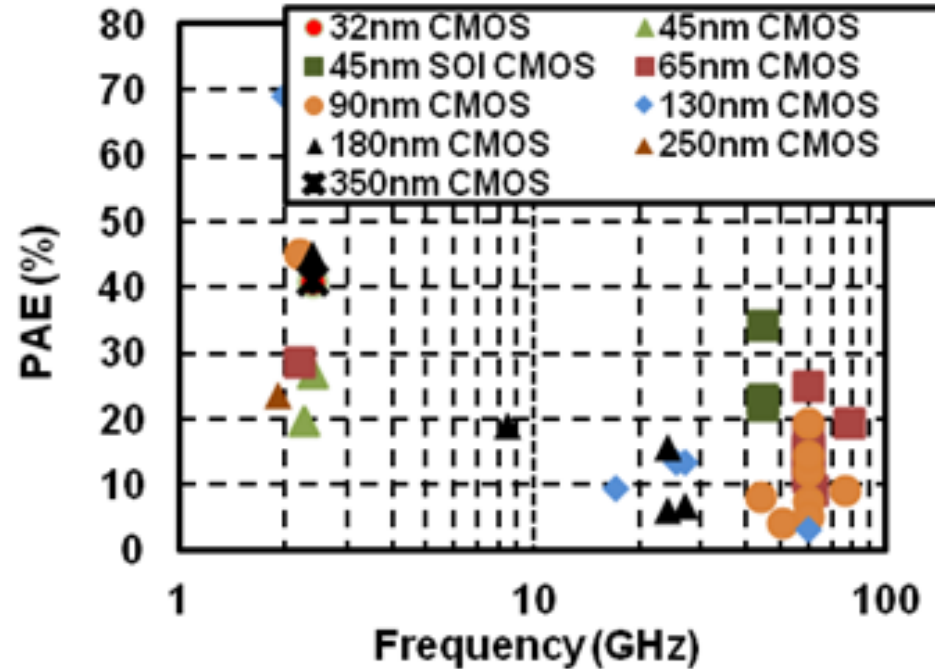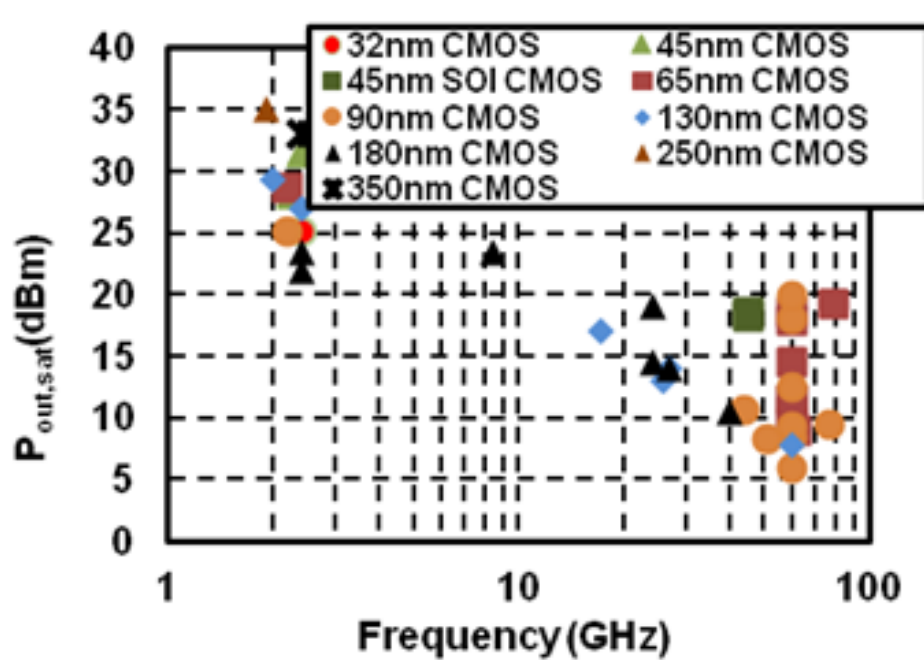


- Output power and PAE degrade drastically at mmwave.
- Efficient unit cell PA design with high output power is challenging.

Can we get a watt of output power in CMOS at mmWave?

Outline


- Motivation
- **Stacking and Switch-mode Operation**
- Large-scale Power Combining
- Linearized High Backoff-Efficiency Power DAC employing
Supply Switching and Dynamic Load Modulation
- Conclusion

Device Stacking in mmWave CMOS PAs

 

42 GHz 4-stack Class A/AB PA

[Dabag, MTT 2012]

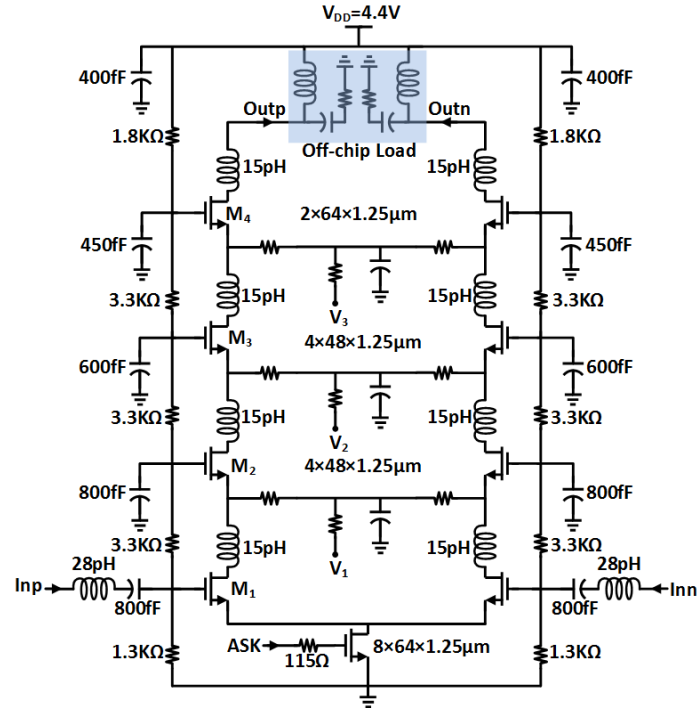


45 GHz 4-stack Class B/AB PA

[Balteanu, RFIC 2012]

- Stacking increases output swing, eliminates the need for output matching to reach a desired output power level.
- Gain increases, thereby improving PAE


Can stacking be employed with switching class PAs?

Conventional Class-E PA Design

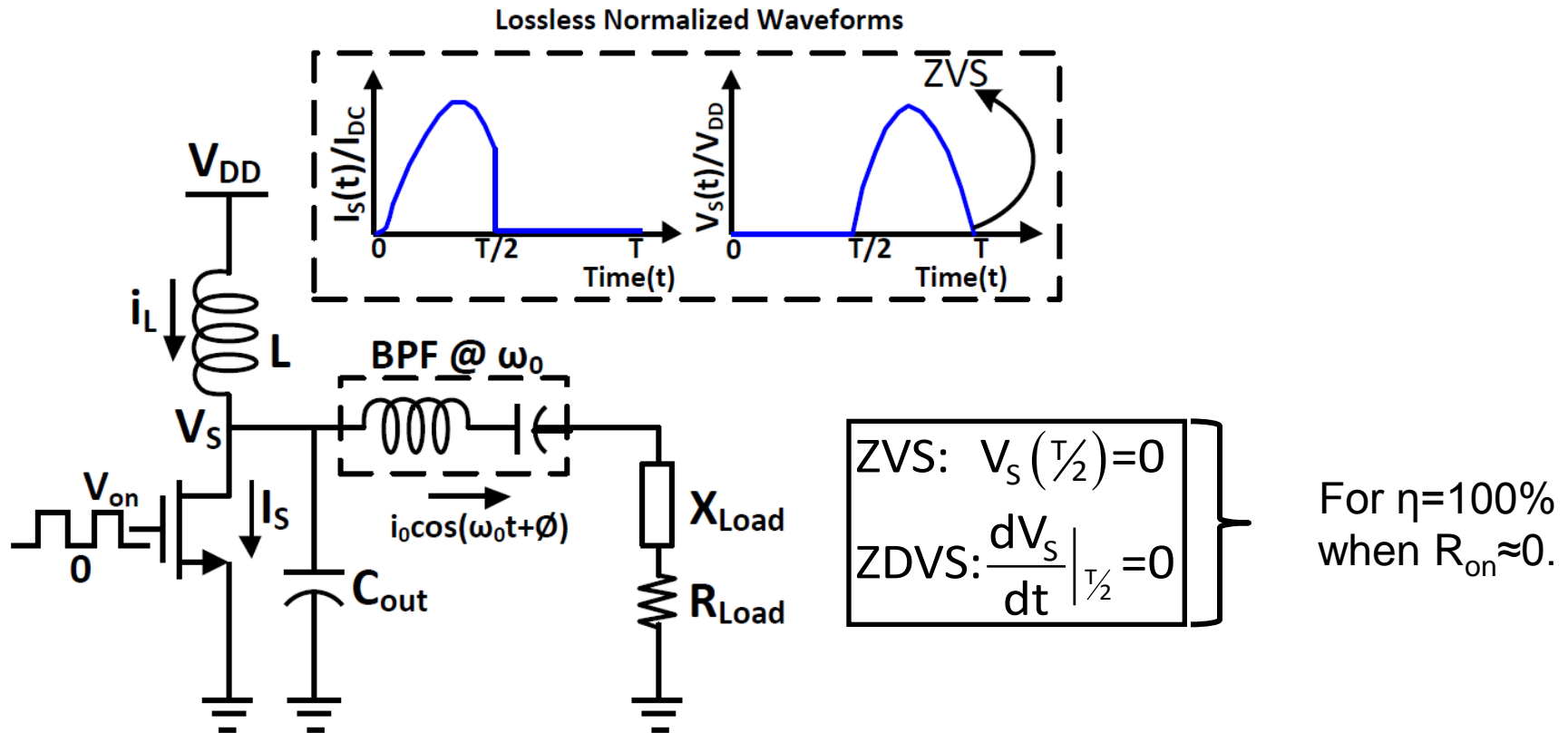


- Conventional Class E design enforces Zero Voltage Switching (ZVS) and Zero-Derivative of Voltage (ZdVS) for ideally 100% efficiency.
- This approach is sub-optimal when the switch and passive components contribute significant loss.

Loss-Aware mmWave Stacked Class-E

 

The stacked devices are assumed to behave like a single switching device with a linearly larger R_{on} and V_{dd} .

Loss-Aware mmWave Stacked Class-E

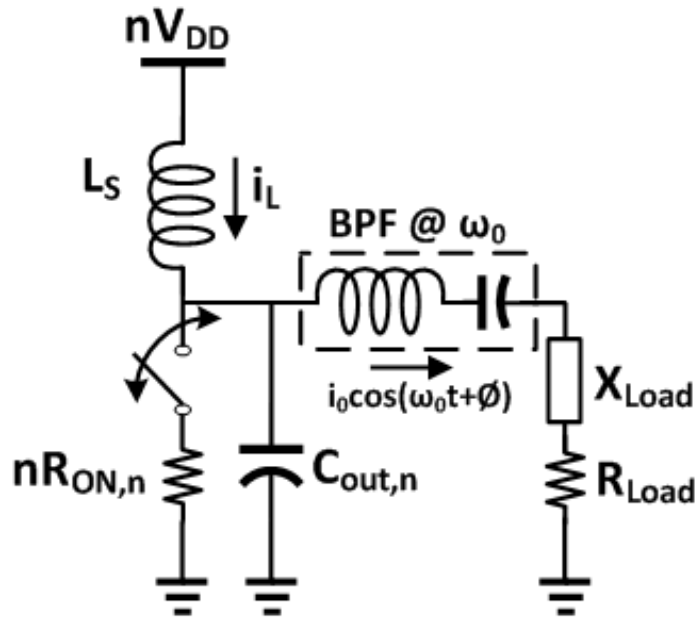



HIGHLIGHTS OF ANALYTICAL FORMULATION*

- Takes finite choke inductance (L_S) into account.
- Takes the effect of switch R_{ON} into account formally (but assumes $R_{ON} \ll 1/\omega C_{out}$).
- Takes into account passive loss.
- Takes into account input drive power.
- Load impedance is not chosen for Class E switching conditions (ZVS/ZdVS) but rather are varied to optimize PAE.
- Analytical equivalent to load-pull simulations.
- Provides a starting point for design optimization.

Loss-Aware mmWave stacked Class-E design methodology formally takes into account several mmWave non-idealities (device loss, input drive power, passive loss).

**Anandaroop Chakrabarti and Harish Krishnaswamy, "An Improved Analysis and Design Methodology for RF Class-E Power Amplifiers with Finite DC-feed Inductance and Switch On-Resistance," 2012 IEEE ISCAS.*

Device Stacking in 45nm SOI at 45GHz

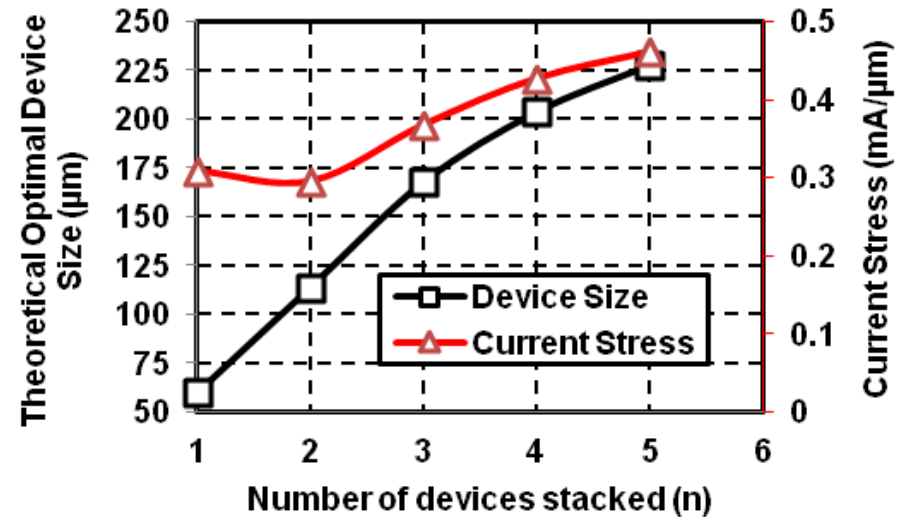
 


- $P_{out} > 20\text{dBm}$ can be achieved by stacking without drastic penalty in PAE.
- Device size and current stress determine the maximum number of devices that can be stacked.
- The graphs represent fundamental limits on achievable performance in stacked CMOS Class-E-like PAs.

Chakrabarti, A; Krishnaswamy, H., "High-Power High-Efficiency Class-E-Like Stacked mmWave PAs in SOI and Bulk CMOS: Theory and Implementation," *IEEE Transactions on Microwave Theory and Techniques*, Aug. 2014

Stacking versus Power Combining



2-stack PA

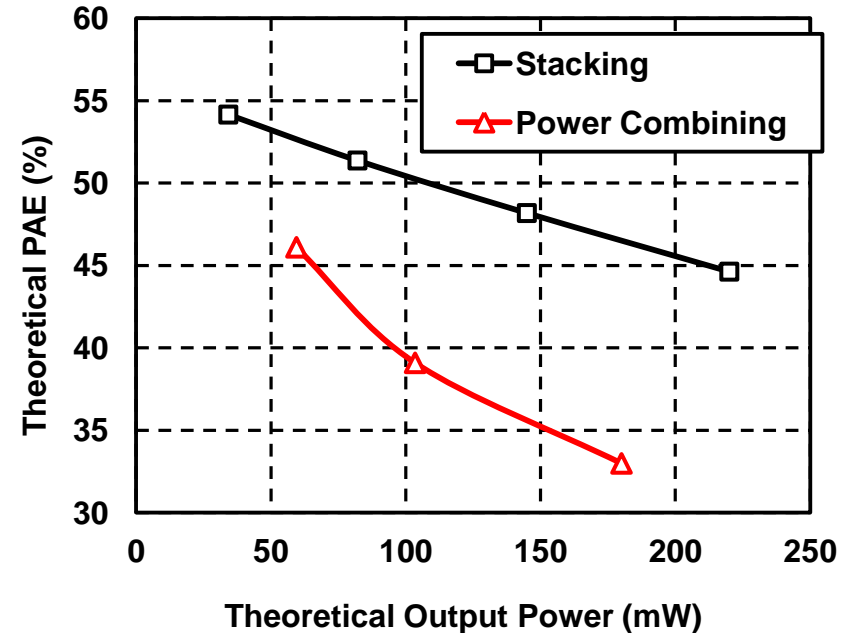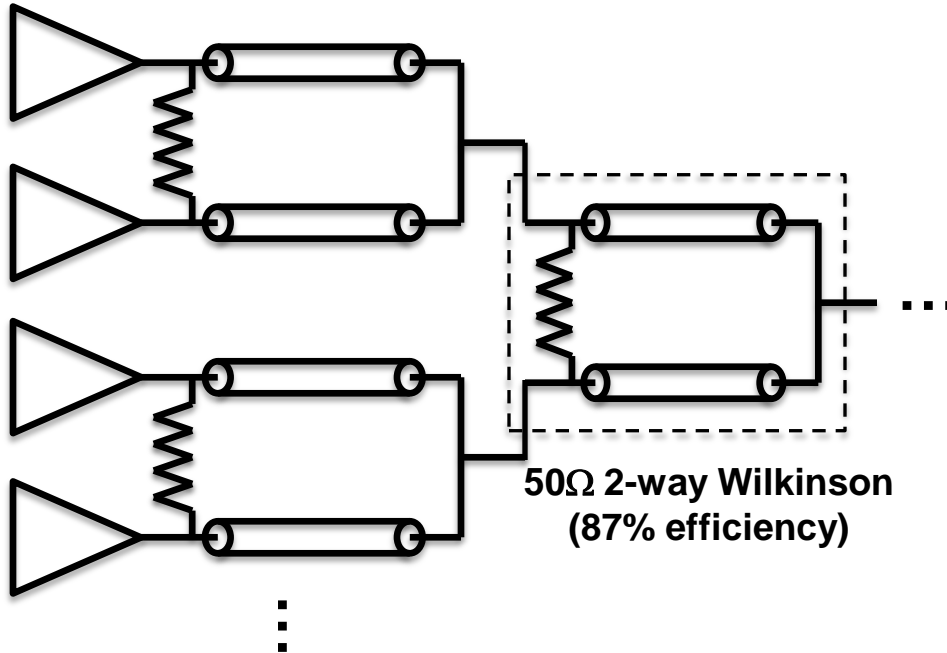

- Series stacking is compared with the power combining of multiple 2-stack Class-E-like PAs using a tree of 2-way 50Ω Wilkinson combiners.
- Series stacking enables significantly higher efficiency for the same output power level.

Chakrabarti, A; Krishnaswamy, H., "High-Power High-Efficiency Class-E-Like Stacked mmWave PAs in SOI and Bulk CMOS: Theory and Implementation," *IEEE Transactions on Microwave Theory and Techniques*, Aug. 2014



Stacking vs. Impedance Transformation

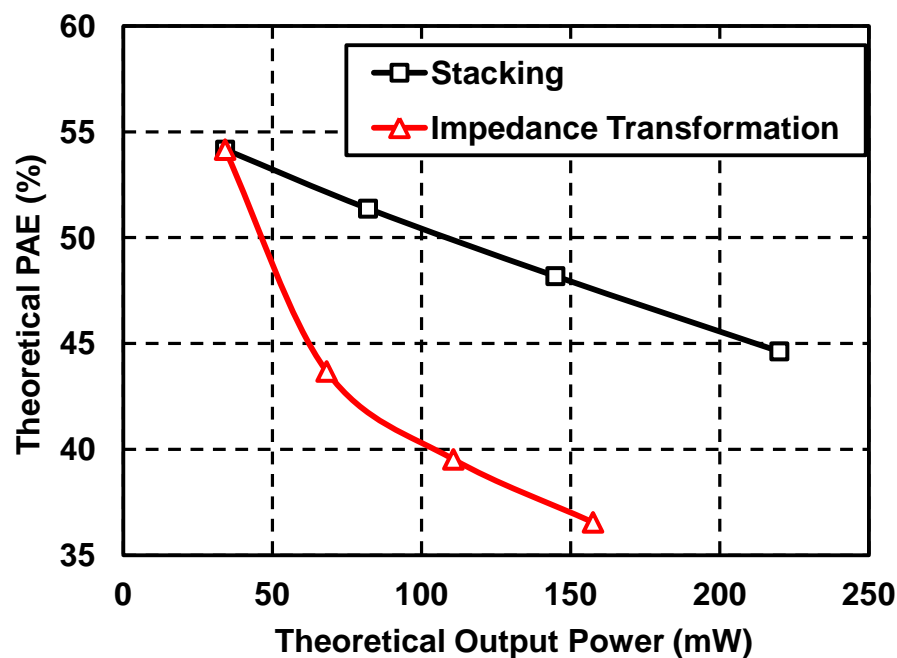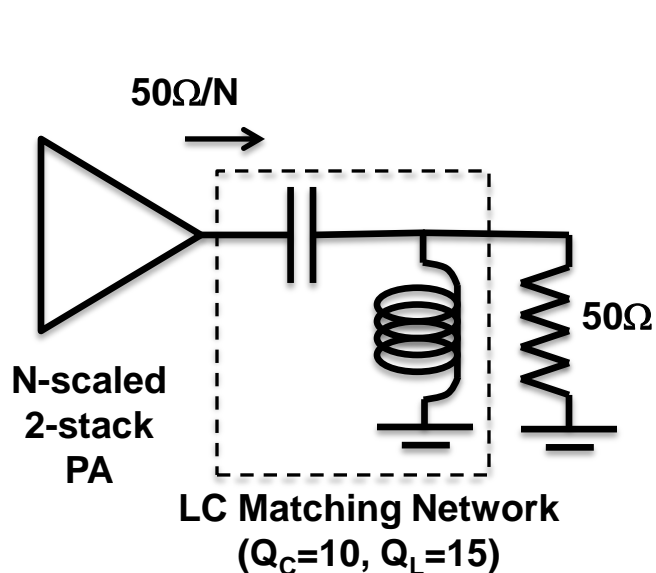

- Series stacking is compared with the use of LC impedance transformers in conjunction with scaled 2-stack Class-E-like PAs.
- Series stacking enables significantly higher efficiency for the same output power level.

Chakrabarti, A; Krishnaswamy, H., "High-Power High-Efficiency Class-E-Like Stacked mmWave PAs in SOI and Bulk CMOS: Theory and Implementation," *IEEE Transactions on Microwave Theory and Techniques*, Aug. 2014



2-stacked 65nm Diff. Class E PA

 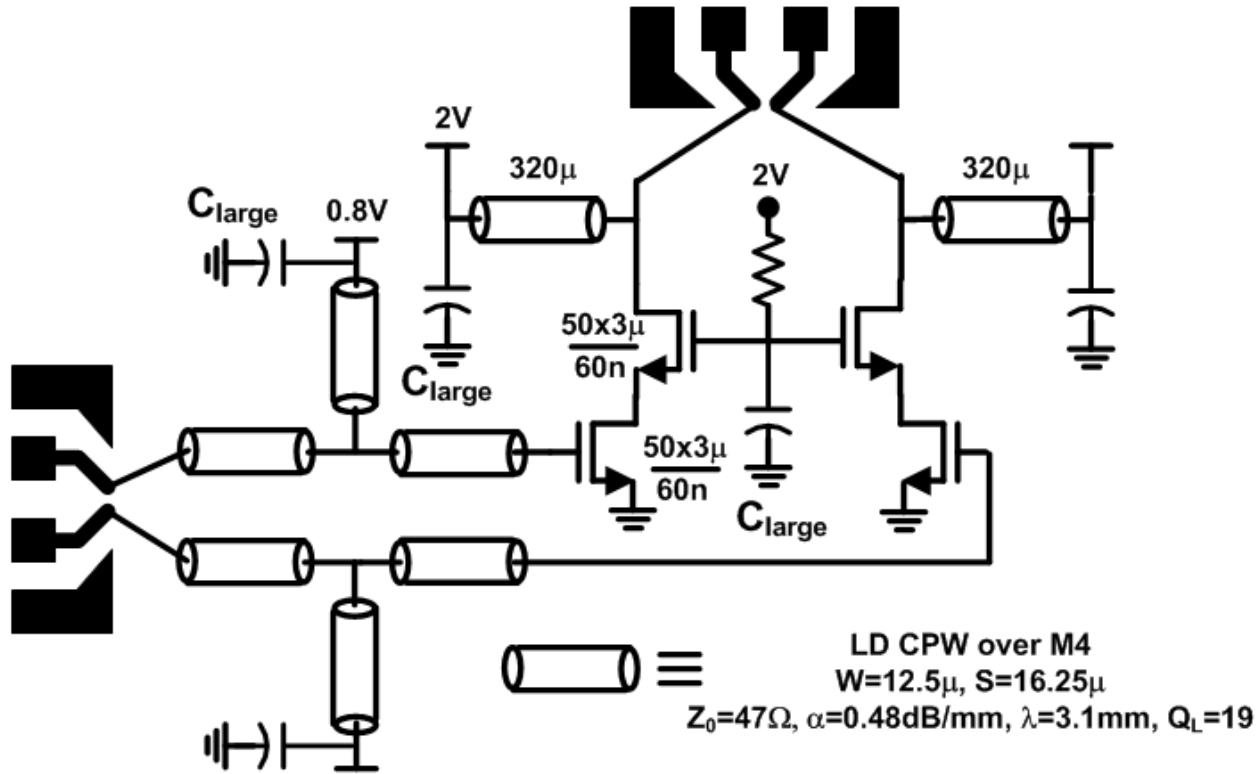

$P_{\text{sat}} = 18.2\text{dBm}$ $PAE_{\text{max}} = 28\%$
--

Pseudo-differential, 2-stacked unit PA is designed based on the finite-choke, Class E design methodology.

2-stacked 45nm SOI Class E PA

 
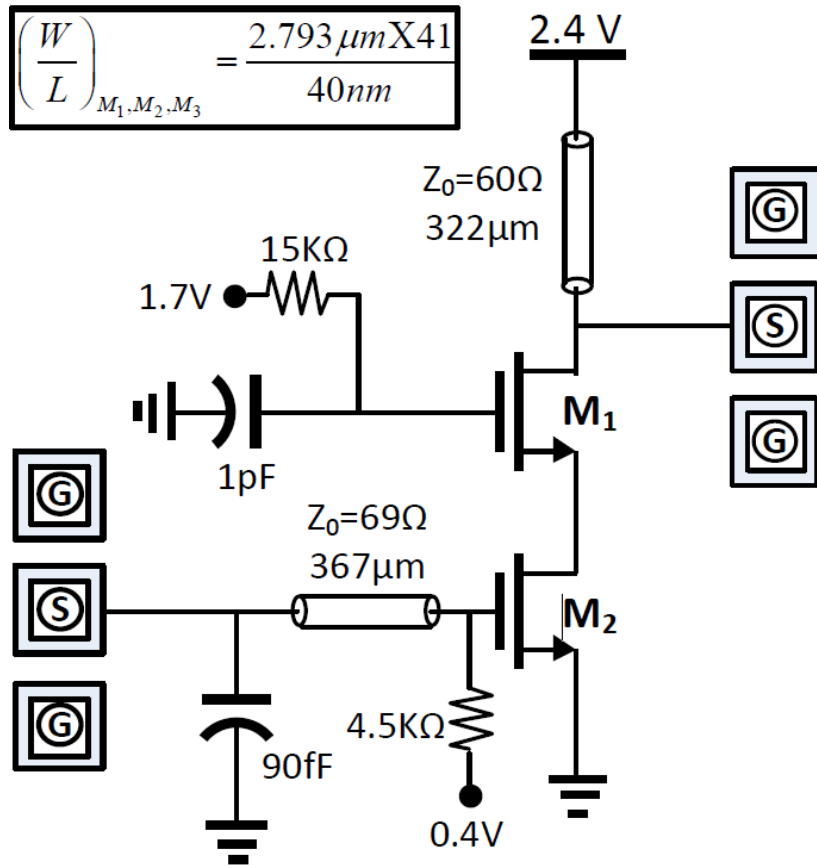


$P_{\text{sat}} = 17.6\text{dBm}$
 $\text{PAE}_{\text{max}} = 35\%$

Single-Ended 2-stacked Class E PA designed based on the Loss-Aware Millimeter-Wave Stacked-Class-E design methodology.

Anandaroop Chakrabarti and Harish Krishnaswamy, "High Power, High Efficiency Stacked mmWave Class-E-like Power Amplifiers in 45nm SOI CMOS," 2012 IEEE Custom Integrated Circuits Conference.

4-stacked 45nm SOI Class E PA




 
 


$P_{\text{sat}} = 20.3\text{dBm}$
 $\text{PAE}_{\text{max}} = 20\%$

Single-Ended 4-stacked Class E PA designed based on the Loss-Aware Millimeter-Wave Stacked-Class-E design methodology.

Anandaroop Chakrabarti and Harish Krishnaswamy, "High Power, High Efficiency Stacked mmWave Class-E-like Power Amplifiers in 45nm SOI CMOS," 2012 IEEE Custom Integrated Circuits Conference.

Packaged 45GHz CMOS PAs

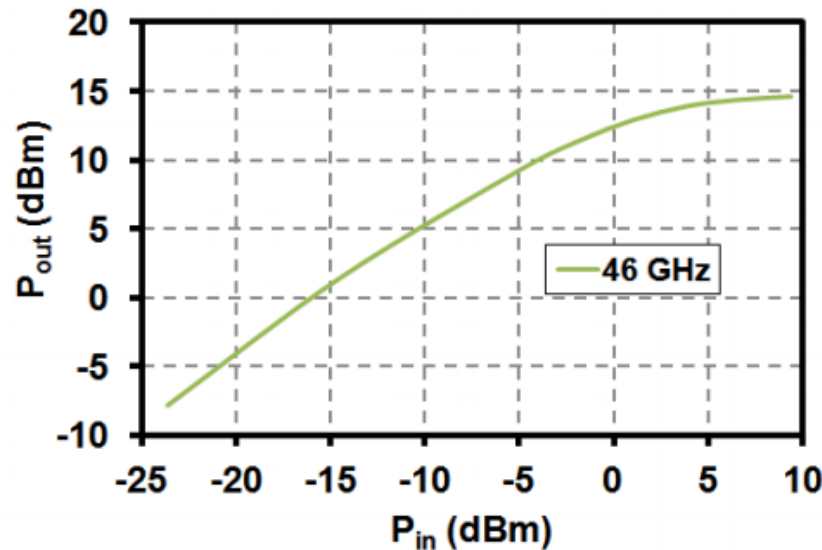    


Packaged and connectorized Q-band stacked 45nm SOI CMOS Class-E-like PA has been transitioned to Northrop Grumman for insertion into a SATCOM demo.

Outline

- Motivation
- Stacking and Switch-mode Operation
- **Large-scale Power Combining**
- Linearized High Backoff-Efficiency Power DAC employing
Supply Switching and Dynamic Load Modulation
- Conclusion


On-Chip Power Combining Challenges

Transformer Combining

 


- Asymmetric input impedance due to parasitics results in destructive combining and stability challenges.

Current Combining

 


- Increased load reduces power generated by each PA – no power combining benefit.

Wilkinson Combining

 

- Cascading 2:1 Wilkinsons results in increased loss.
- N:1 Wilkinsons are challenging due to high Z_0 required.

8-way Lumped $\lambda/4$ Power Combiner

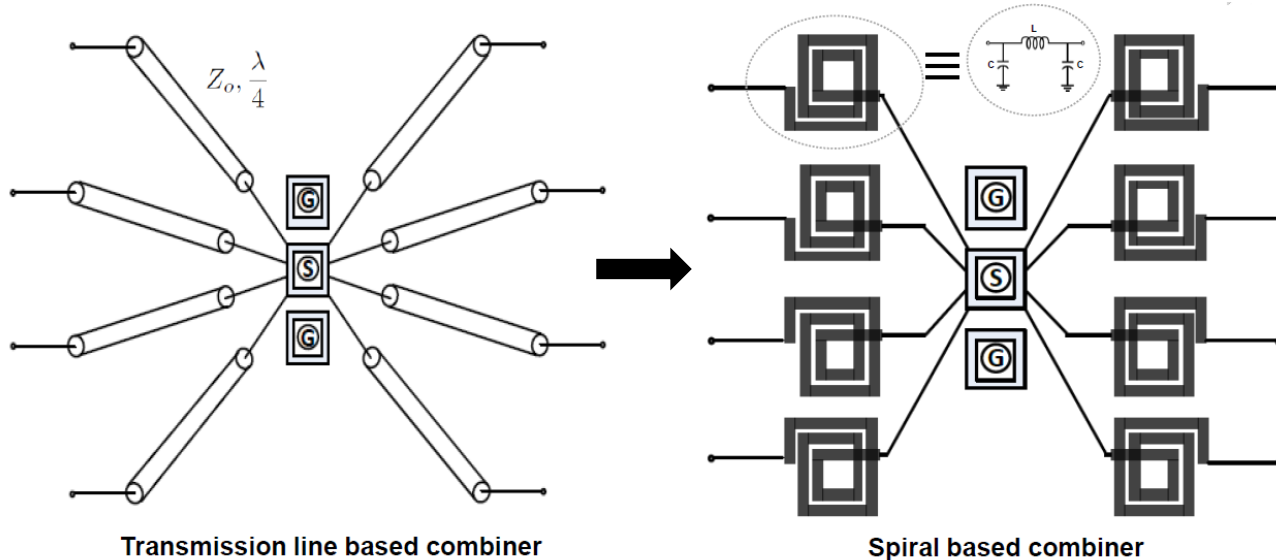

$$Z_o(n) = 50\sqrt{n}$$



$$Z_o(8) = 141.421\Omega$$

$$Z_o(n) = \sqrt{\frac{L(n)}{C(n)}}; \omega = \frac{1}{\sqrt{L(n)C(n)}}$$

$$L(8)|_{45GHz} = 0.5nH; C(8)|_{45GHz} = 25fF$$


- Large-scale 8-way power combining is used to enhance output power.
- Lumped equivalents of quarter-wave lines are used to easily achieve the necessary high Z_o .

Combiner Performance

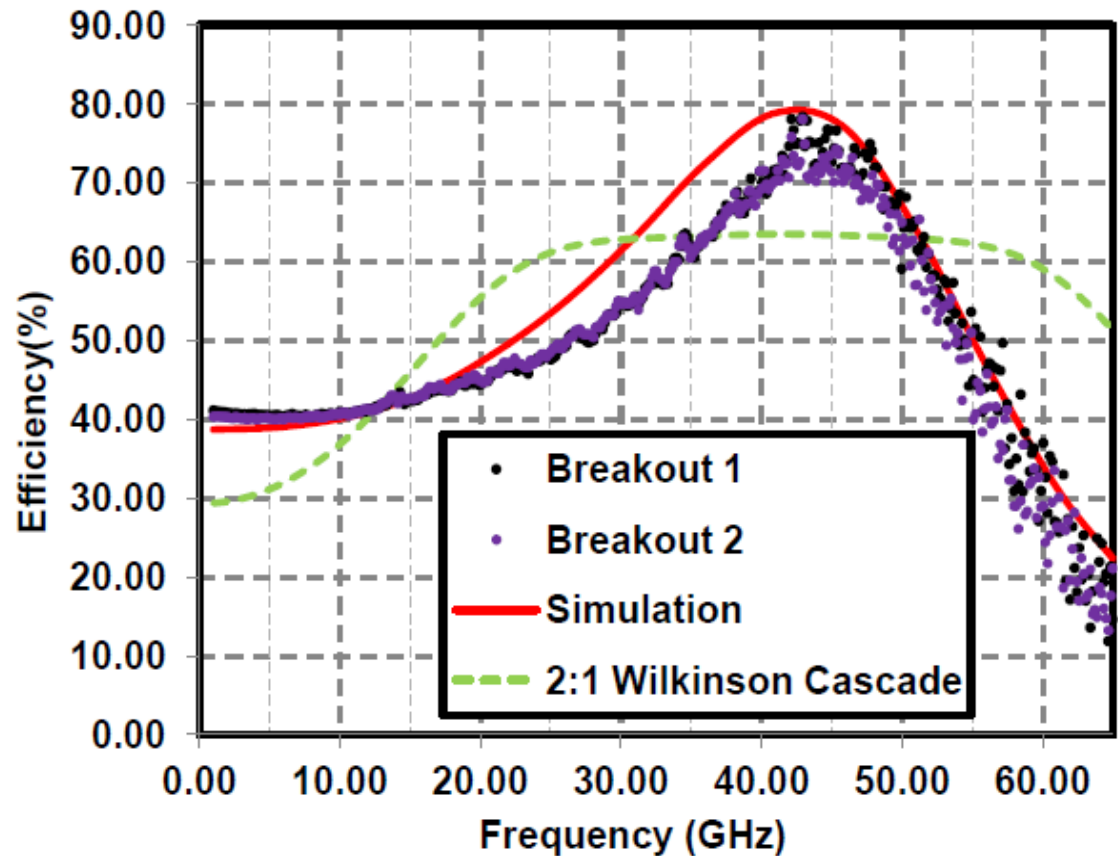 


- Measurements closely correspond with EM simulations.
- Achieves **78%** peak efficiency in contrast to an 8-way 2:1 Wilkinson cascade which achieves only 63% at 45GHz.

45GHz 45nm SOI Watt-class PA

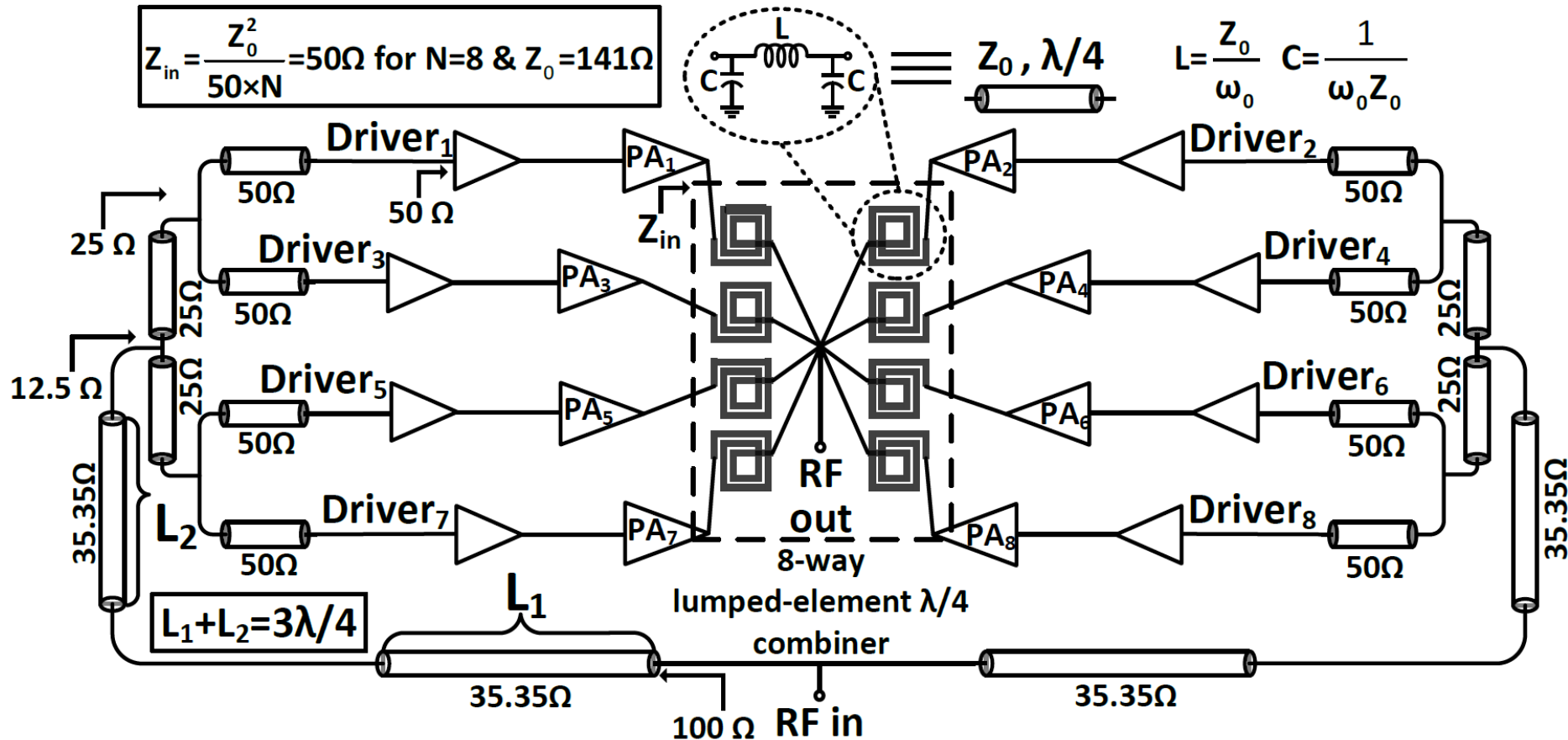


Eight unit cells (a two-stacked driver + a four-stacked main PA) power-combined using the eight-way lumped-element $\lambda/4$ combiner.

45GHz 45nm SOI Watt-class PA

 


Ritesh Bhat, Anandaroop Chakrabarti and Harish Krishnaswamy, "Large-Scale Power-Combining and Linearization in Watt-Class mmWave CMOS Power Amplifiers," 2012 IEEE RFIC Symposium.

Watt-class PA S-Parameter Measurement

 


Peak $S_{21} = 19.4\text{dB}$ at 50GHz with a 3dB BW of 13GHz.

Watt-Class PA Large-Signal Performance

 


Peak output power of $>27\text{dBm}$ and -1dB flatness is observed in $P_{out,sat}$ and $P_{out,-1\text{dB}}$ from 33-46GHz.

Preliminary RF Probed Stress Test

 

- The PA is driven at the $P_{out,sat}$ drive level for 12.5 hours on a probe station.
- Variations seen in output power and efficiency are small.


Comparison with CMOS mmWave PAs

 


Outline

- Motivation
- Stacking and Switch-mode Operation
- Large-scale Power Combining
- Linearized High Backoff-Efficiency Power DAC employing
Supply Switching and Dynamic Load Modulation
- Conclusion

Motivation

 

 
Probability density function of the amplitude of a pulse shaped 64 QAM signal



- Power amplifiers have a linearity vs. efficiency tradeoff.
- High efficiency under back-off is essential to support complex modulation schemes.


Can linearity, large-scale power combining and better than Class B back-off efficiency co-exist?

Power DAC Approach

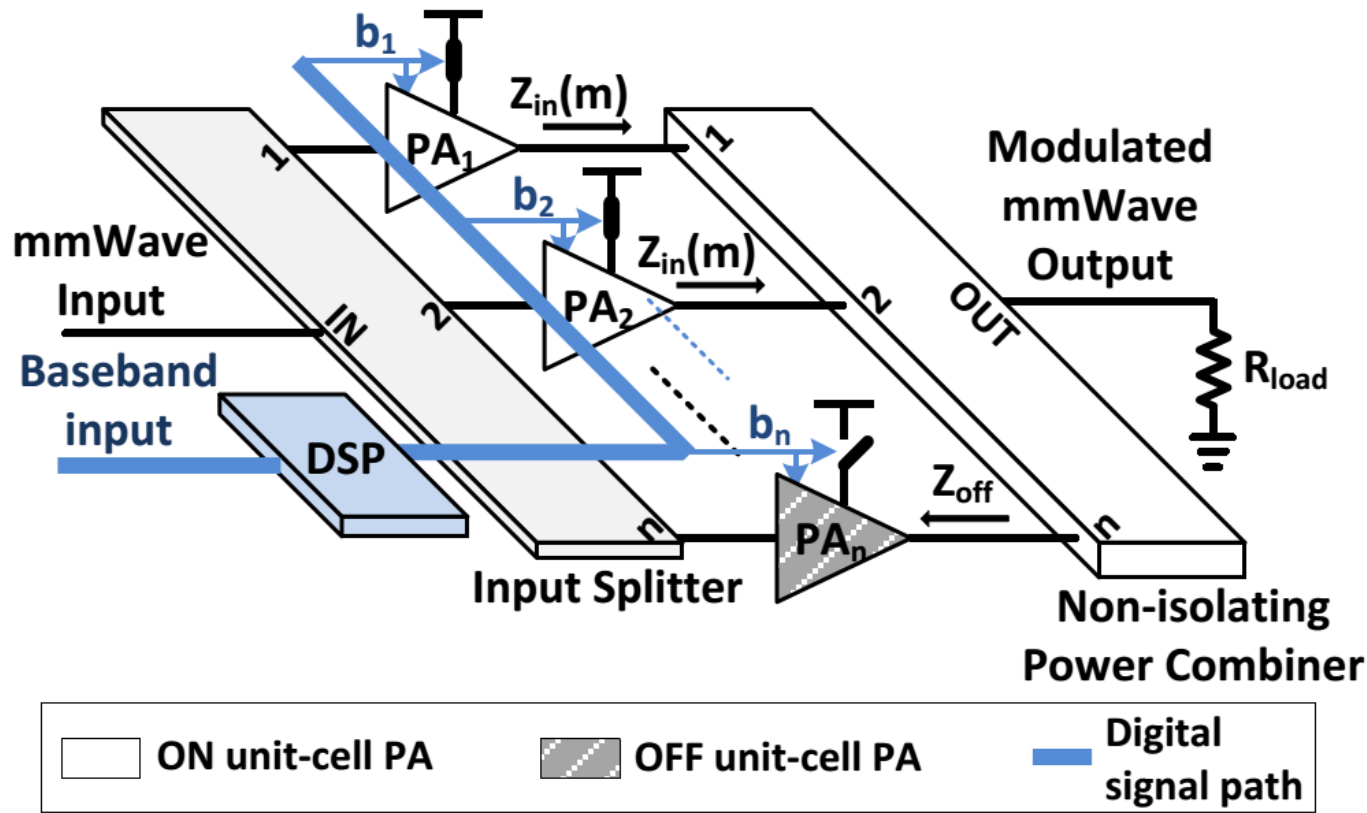



- Supply-switched power-combined DAC for multi-bit resolution & high average efficiency .
- Load modulation using non-isolating combiner facilitates linear DAC profile.

3-bit Digital-to-mmWave PA Array

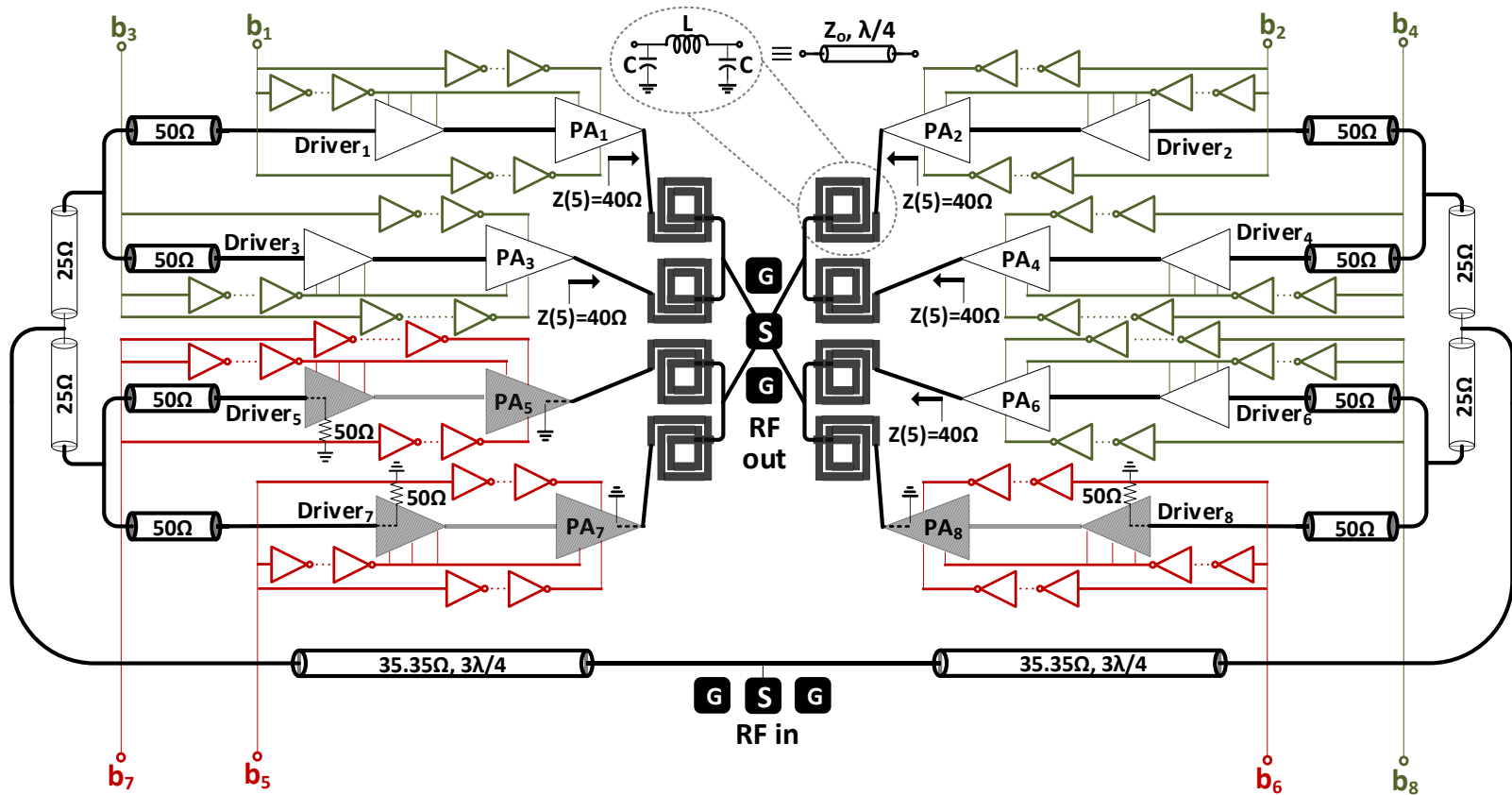

First linearizing PA architecture at mmWave frequencies that simultaneously employs large-scale power combining for higher P_{out} , PA supply switching for higher efficiency under back-off, and load-modulation for linearization of switching PAs.


Supply-switched Class-E-like PA

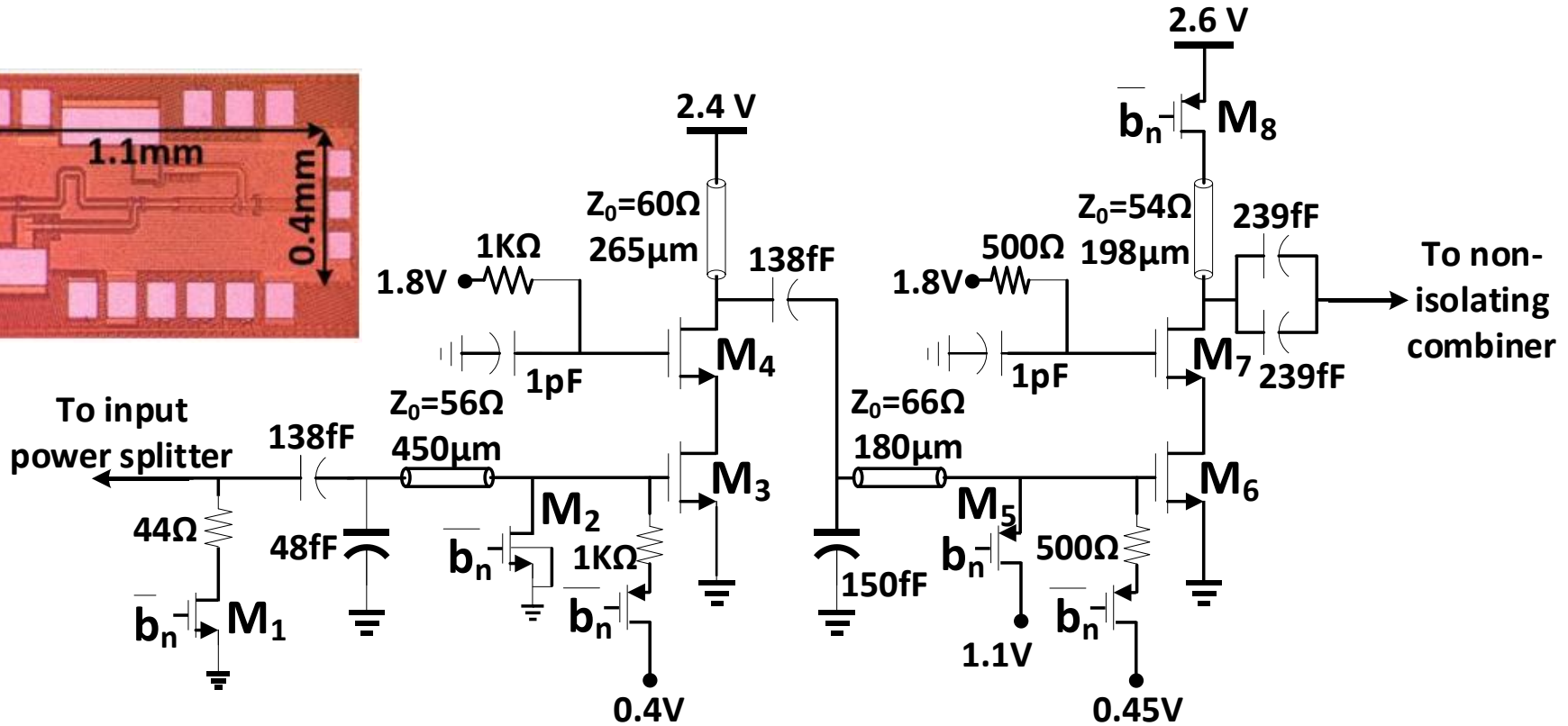 

- 1-bit supply-switched power DAC cell in 45nm SOI CMOS.
- 2-stacked Class-E PA unit cell augmented with digital switches to facilitate high-speed turn-on/turn-off.

Andaroop Chakrabarti and Harish Krishnaswamy, "Design Considerations for Stacked Class-E-like mmWave HighSpeed Power DACs in CMOS," 2013 IEEE International Microwave Symposium.

1-bit Cell 1Gbps OOK Meas. @ 47GHz

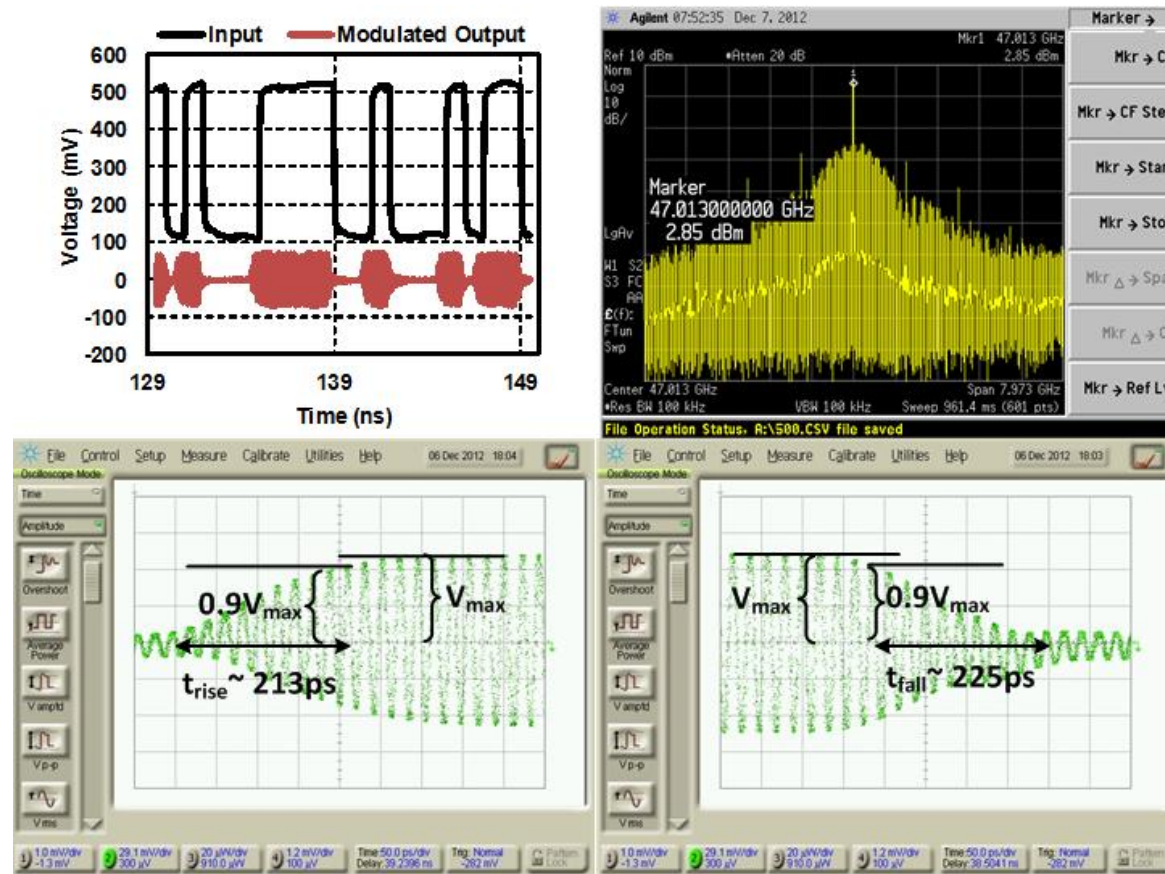


Supply-switched unit cell can be turned on and off at ~ 1 GHz rate.

Anandaroop Chakrabarti and Harish Krishnaswamy, "Design Considerations for Stacked Class-E-like mmWave HighSpeed Power DACs in CMOS," 2013 IEEE International Microwave Symposium.

Operation of the Architecture

$$Z_{in} = Z_0^2 / (50xm) = 25\Omega$$

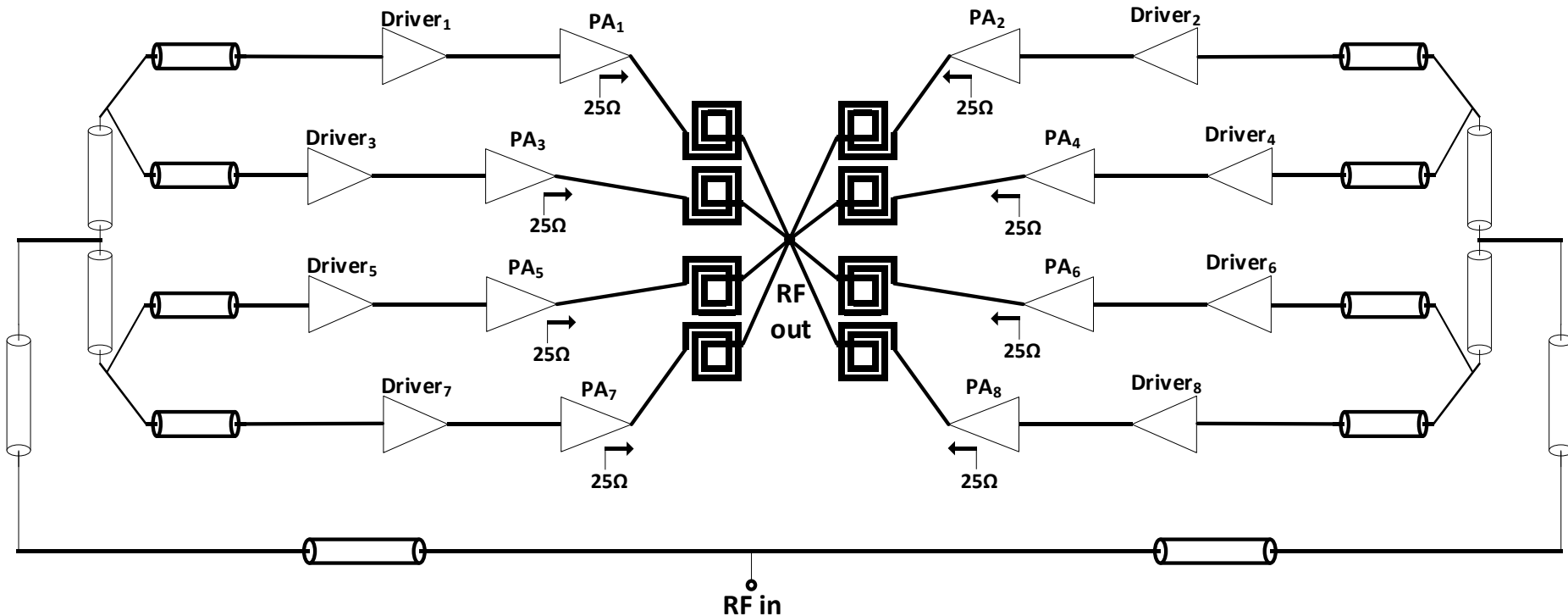


$$P_{out,unit} \propto \frac{V_{DD}^2}{R_L}$$

$$P_{out,total} \propto m \times \frac{V_{DD}^2}{Z_0^2 / (mR_0)} \propto m^2 \frac{V_{DD}^2}{Z_0^2 / (R_0)}$$

Operation of the Architecture
 
$$Z_{in} = Z_0^2 / (50xm) = 28.57\Omega$$




$$P_{out,unit} \propto \frac{V_{DD}^2}{R_L}$$

$$P_{out,total} \propto m \times \frac{V_{DD}^2}{Z_0^2 / (mR_0)} \propto m^2 \frac{V_{DD}^2}{Z_0^2 / (R_0)}$$

Operation of the Architecture
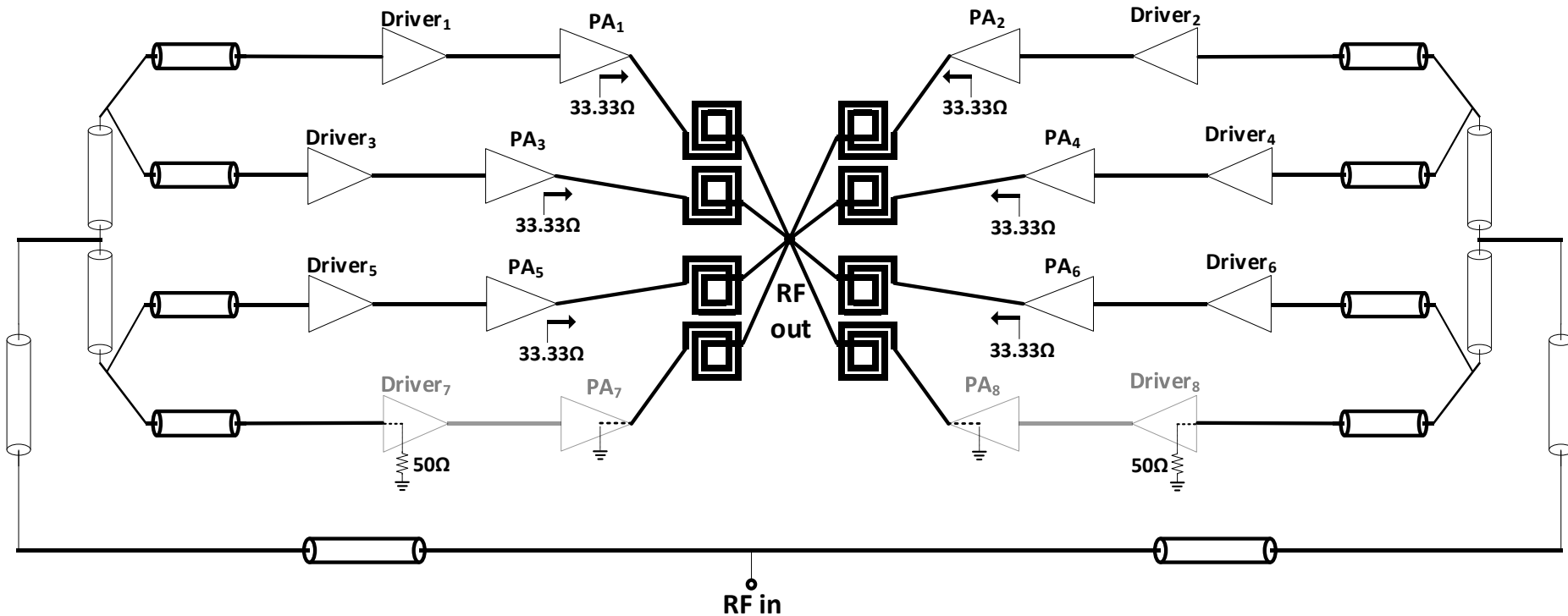
$$Z_{in} = Z_0^2 / (50xm) = 33.33\Omega$$




$$P_{out,unit} \propto \frac{V_{DD}^2}{R_L}$$

$$P_{out,total} \propto m \times \frac{V_{DD}^2}{Z_0^2 / (mR_0)} \propto m^2 \frac{V_{DD}^2}{Z_0^2 / (R_0)}$$

Operation of the Architecture

$$Z_{in} = Z_0^2 / (50xm) = 40\Omega$$

 


$$P_{out,unit} \propto \frac{V_{DD}^2}{R_L}$$

$$P_{out,total} \propto m \times \frac{V_{DD}^2}{Z_0^2 / (mR_0)} \propto m^2 \frac{V_{DD}^2}{Z_0^2 / (R_0)}$$

Operation of the Architecture

$$Z_{in} = Z_0^2 / (50xm) = 50\Omega$$

 


$$P_{out,unit} \propto \frac{V_{DD}^2}{R_L}$$

$$P_{out,total} \propto m \times \frac{V_{DD}^2}{Z_0^2 / (mR_0)} \propto m^2 \frac{V_{DD}^2}{Z_0^2 / (R_0)}$$

Operation of the Architecture
 
$$Z_{in} = Z_0^2 / (50xm) = 66.66\Omega$$




$$P_{out,unit} \propto \frac{V_{DD}^2}{R_L}$$

$$P_{out,total} \propto m \times \frac{V_{DD}^2}{Z_0^2 / (mR_0)} \propto m^2 \frac{V_{DD}^2}{Z_0^2 / (R_0)}$$

Operation of the Architecture

$$Z_{in} = Z_0^2 / (50xm) = 100\Omega$$

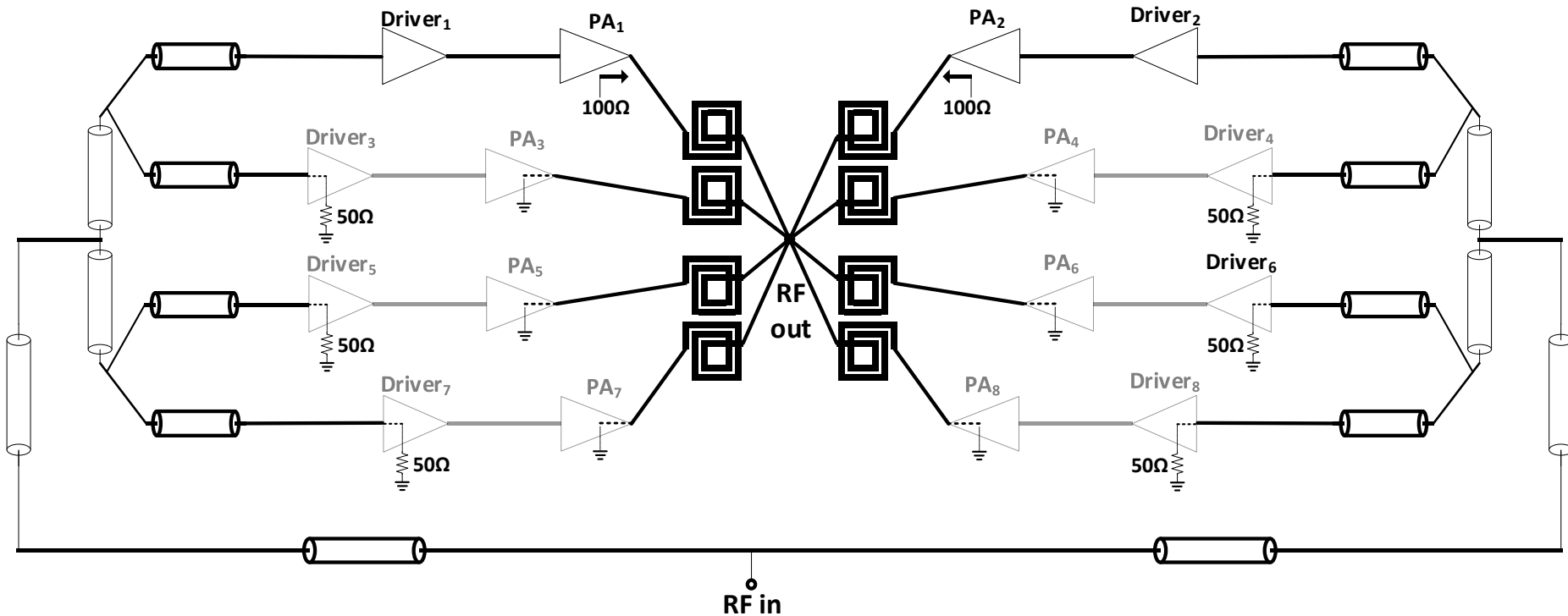


$$P_{out,unit} \propto \frac{V_{DD}^2}{R_L}$$

$$P_{out,total} \propto m \times \frac{V_{DD}^2}{Z_0^2 / (mR_0)} \propto m^2 \frac{V_{DD}^2}{Z_0^2 / (R_0)}$$

Operation of the Architecture


$$Z_{in} = Z_0^2 / (50xm) = 200\Omega$$

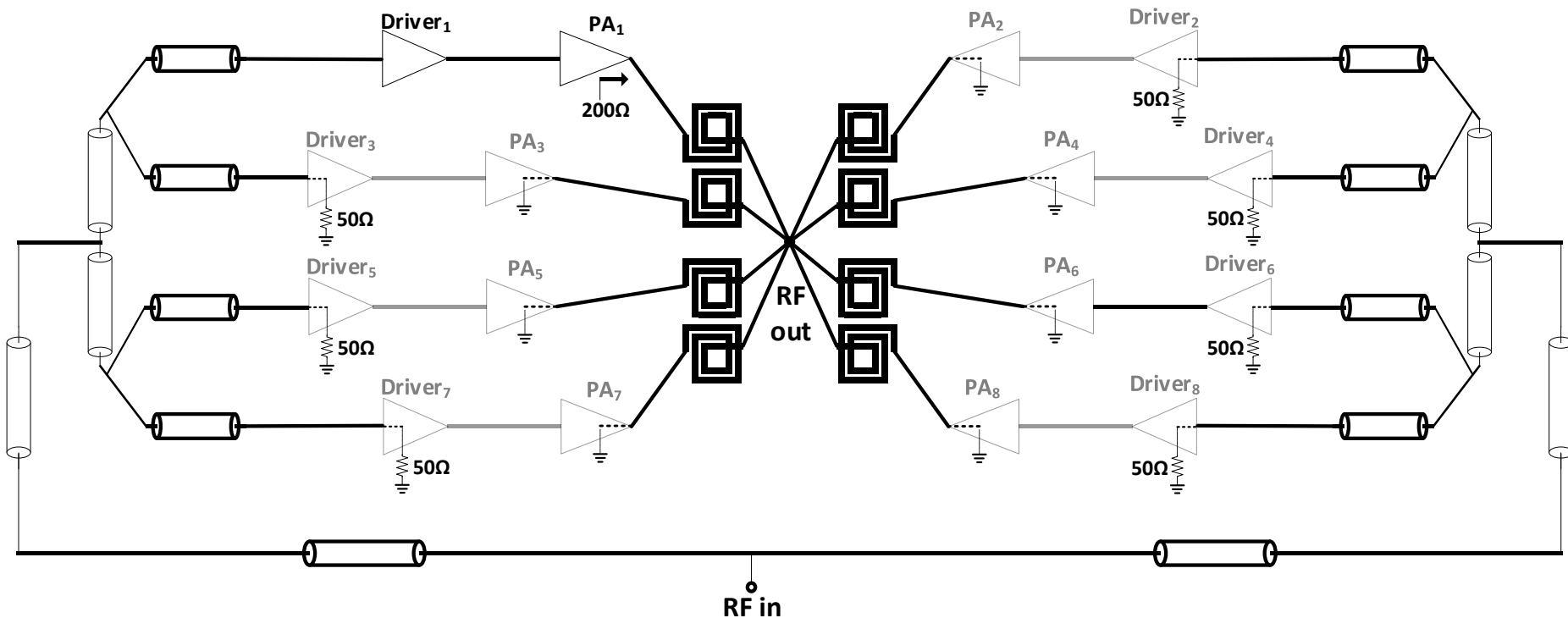

$$P_{out,unit} \propto \frac{V_{DD}^2}{R_L}$$





$$P_{out,total} \propto m \times \frac{V_{DD}^2}{Z_0^2 / (mR_0)} \propto m^2 \frac{V_{DD}^2}{Z_0^2 / (R_0)}$$

3-bit Digital-to-mmWave PA Array

 



Ritesh Bhat, Anandaroop Chakrabarti and Harish Krishnaswamy, "Large-Scale Power-Combining and Linearization in Watt-Class mmWave CMOS Power Amplifiers," 2012 IEEE RFIC Symposium.

Power DAC Output Power and Amplitude

    


System Performance

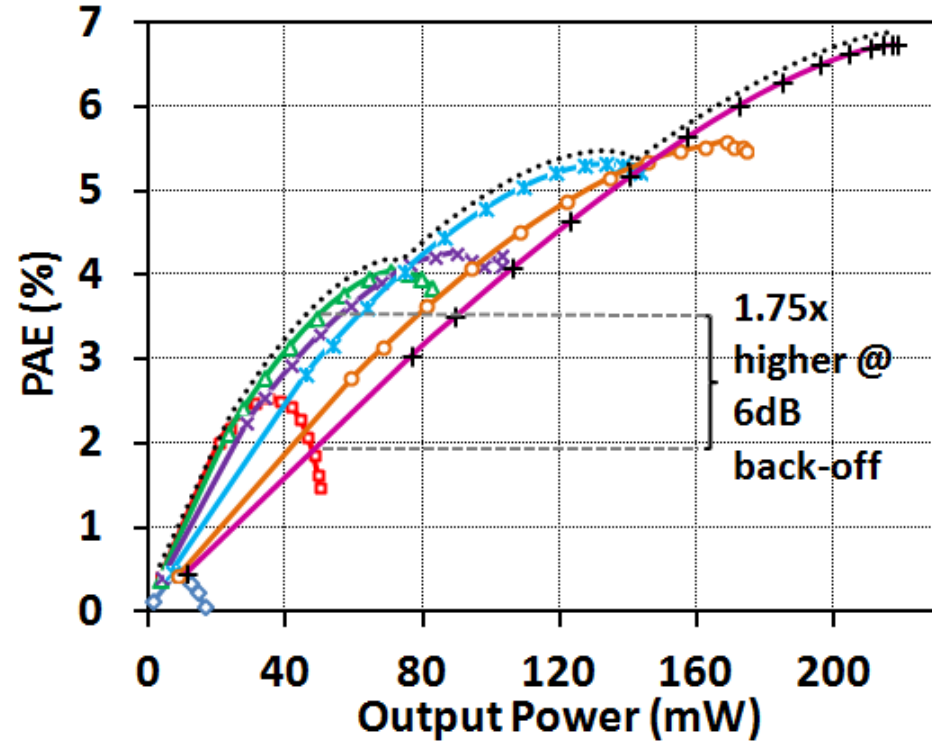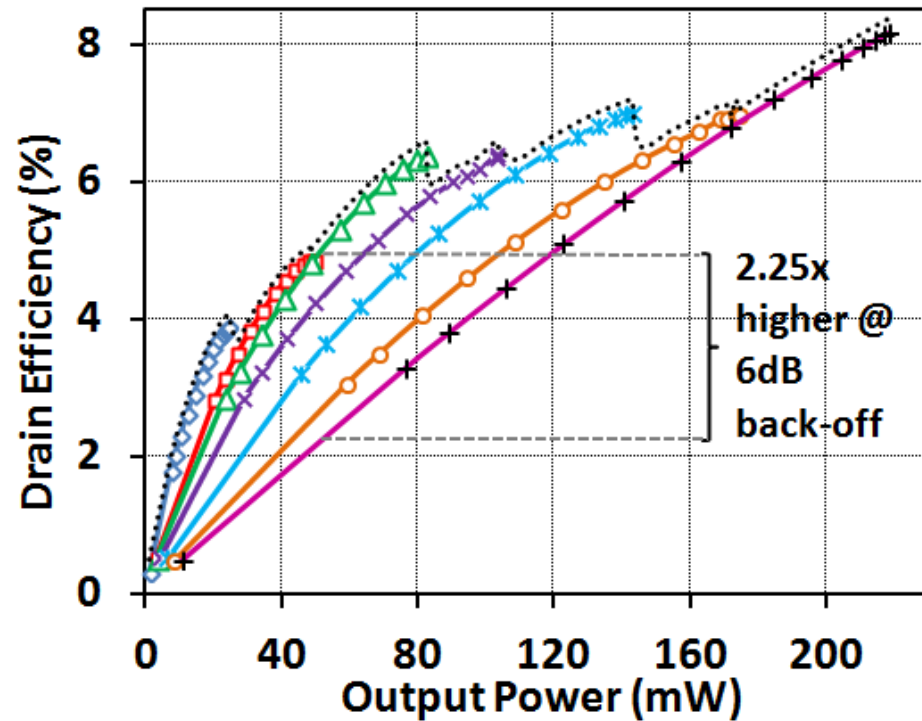—○— m=2 —○— m=3 —△— m=4 —×— m=5 —×— m=6 —○— m=7 —+— m=8 - - Effective System Efficiency



- Measurements show 8.2% peak DE and 6.2% peak PAE.
- A **2.5x** improvement in drain efficiency and a **2x** improvement in PAE at 6dB backoff over the baseline case where all PAs are always kept on.

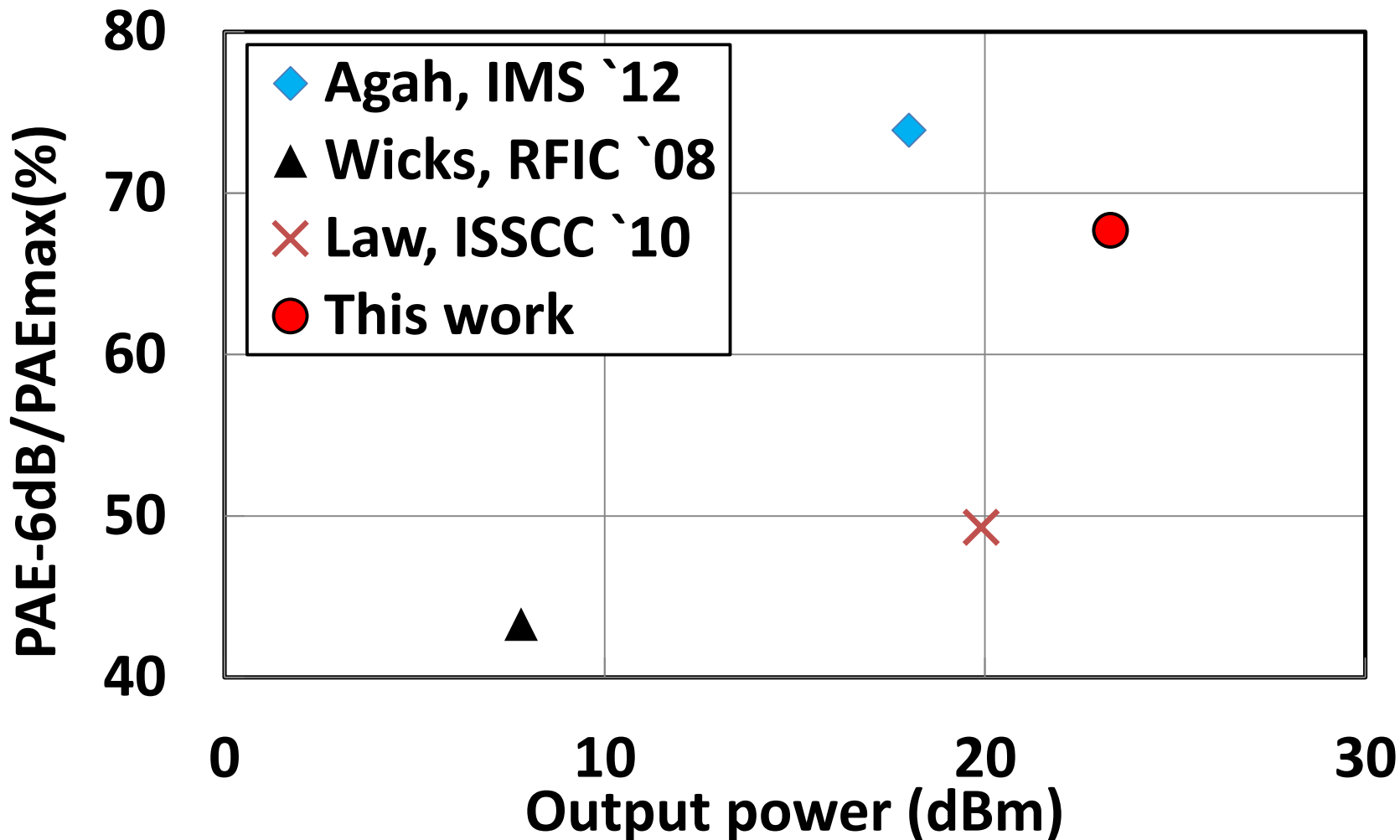Comparison to >20dBm/Linearized CMOS mmWave PAs



Outline

- Motivation
- Stacking and Switch-mode Operation
- Large-scale Power Combining
- Linearized High Backoff-Efficiency Power DAC employing
Supply Switching and Dynamic Load Modulation
- **Conclusion**

Conclusion

- A comprehensive design methodology for stacked mmWave class-E PAs has been demonstrated.
- A low-loss power combining technique is shown which is used in conjunction with stacking to achieve watt-class output power at mmWave in CMOS.
- A direct digital-to-mmWave power DAC architecture which achieves high output power, linearity and back-off efficiency has been developed.
- Future work involving coexistence of high-resolution, linearity, high-power and high-efficiency under back-off is an exciting area of research.

Acknowledgements

- DARPA ELASTx program (Dr. S. Raman and Dr. Dev Palmer) and AFRL (Dr. R. Worley & Dr. P. Watson).
- Kunal Datta, John Roderick and Prof. Hossein Hashemi of USC for valuable discussions.