


# Power Amplifier Classes Based upon Harmonic Approximation and Lumped-element Loading Networks

(Invited Paper)


Ramon A. Beltran, PhD.

UCSD Power Amplifier Symposium

September 2014

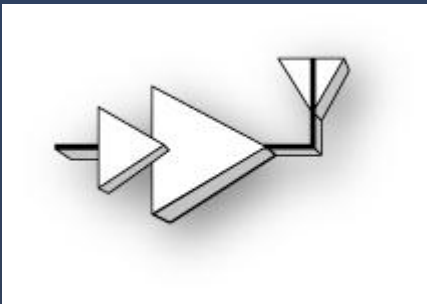

  
**SKYWORKS®**



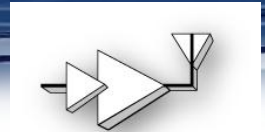


## Outline

- **Class-A, AB, B, C, D, E and F Power Amplifiers**
- **True-transient Operation**
- **Harmonic Approximation**
- **Loading Network Topologies for Compact PAs**
- **Load-Pull Contours and Load Modulation**
- **Summary**


# Ideal Power Amplifier Theory

## Voltage sources and switches

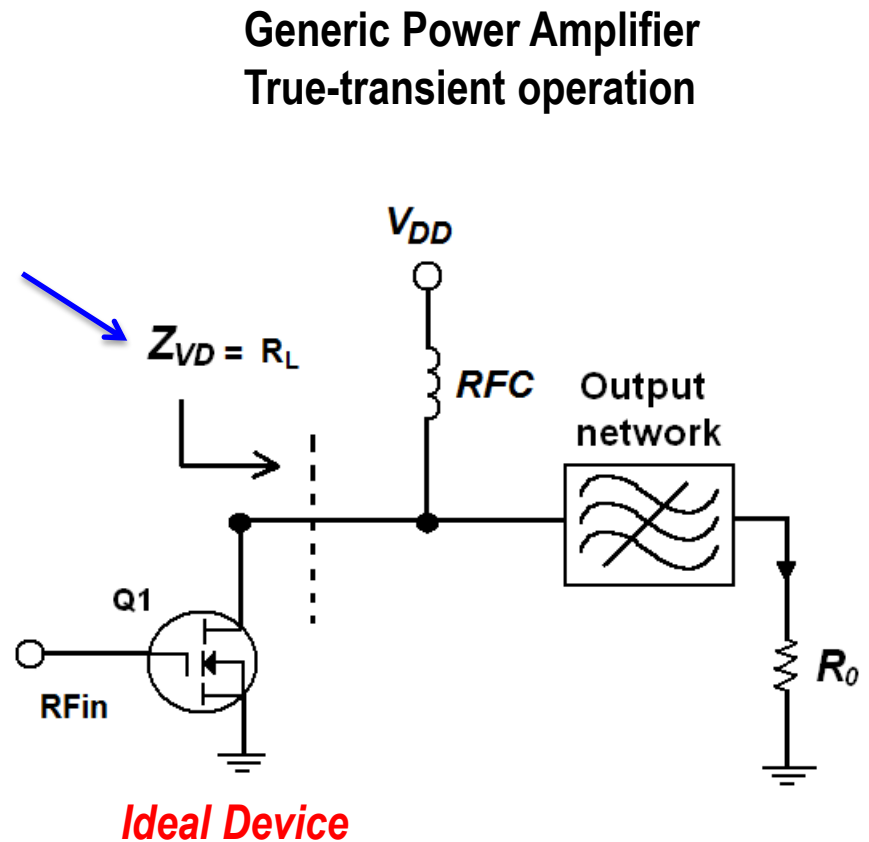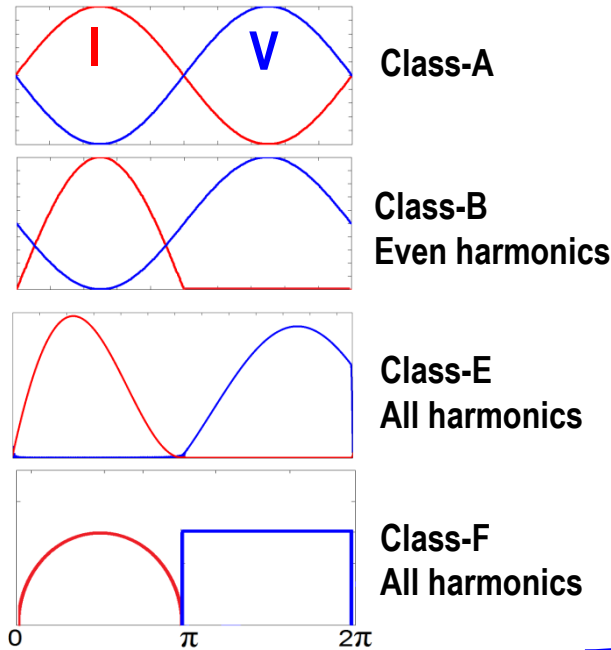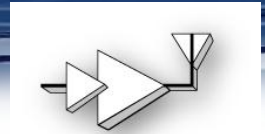
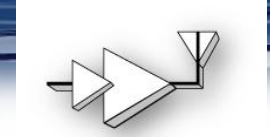
# Power Amplifiers Practical Issues

*Non-ideal voltage sources nor perfect switches*




**Amplifier major practical issues:**

**At high frequency**

**Device package and technology**



**True-transient Operation is not possible**

**Harmonic Approximation can be used**

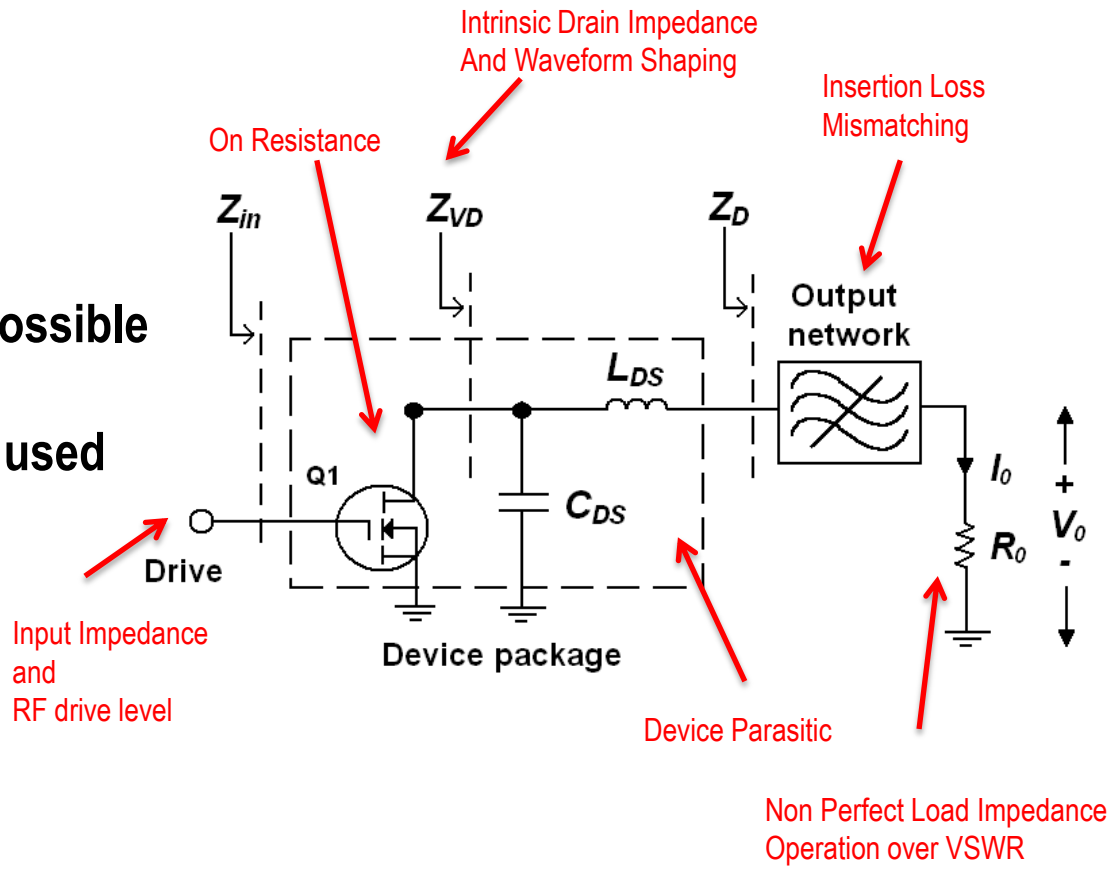


# Ideal Power Amplifier Theory with Parasitics
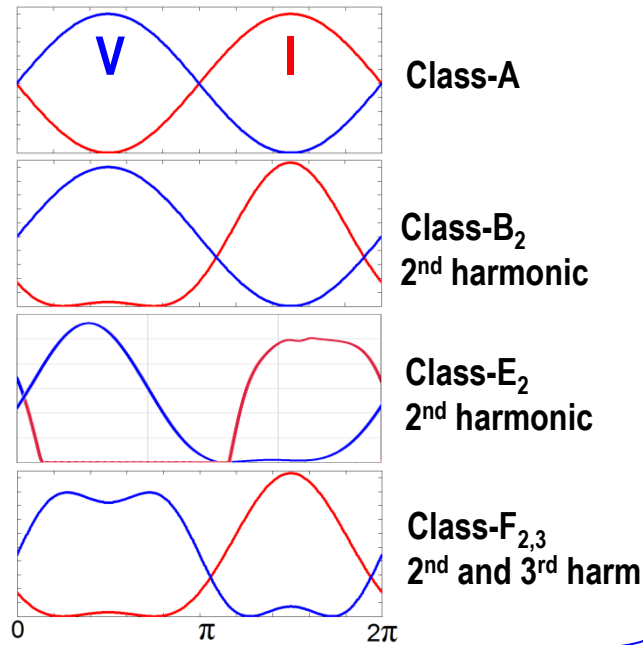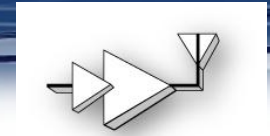
## Non-Ideal voltage sources and switches



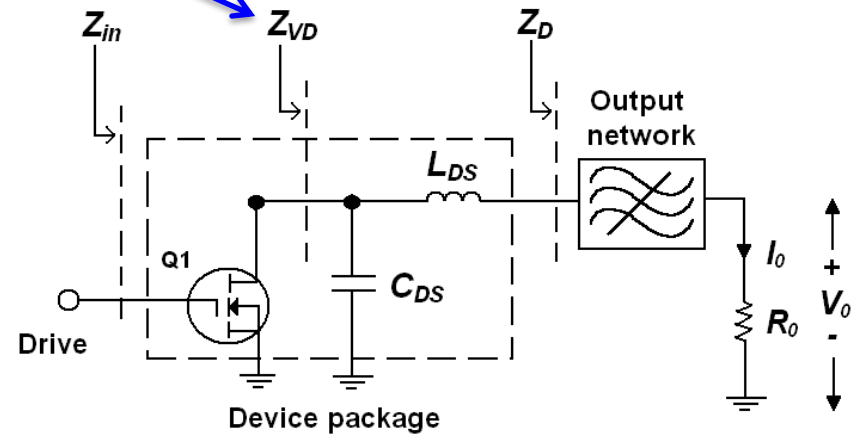
### Power Amplifier with Parasitics Harmonic approximation



# Waveform Coefficients for PA Design

*Efficiency vs. number of harmonics*

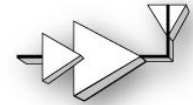


## Efficiency upon combination of harmonics (in %)

HARM	1	3	5	Infinite
1	<b>A</b> 50	57.74	60.33	63.7
2	70.71	<b>F<sub>2,3</sub></b> 81.65	85.32	90.03
4	74.97	86.56	90.45	95.45
Infinite	<b>B</b> 78.5	90.69	94.77	<b>D, E</b> 100

*F. H. Raab, "Maximum efficiency and output of class-F power amplifiers," IEEE Trans. Microwave Theory Tech., vol. 49, no. 6, pp. 1162 - 1166, June 2001.*
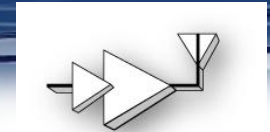
# Amplifier Design by Waveform Factors

Coefficient values upon number of harmonics



$$P_o = \frac{(\gamma_V \cdot V_{eff})^2}{2R_L}$$

$$I_{DC} = \frac{\gamma_V \cdot V_{DD}}{\gamma_I R_L}$$

$$P_{DC} = V_{DD} I_{DC}$$

HARM	$\gamma_V$	$\gamma_I$
1	1	1
2	-----	1.4142
3	1.1547	-----
4	-----	1.0824
5	1.05146	-----
Infinite	1.273	1.571

$$Efficiency = \frac{P_o}{P_{DC}} = \frac{\gamma_V \gamma_I V_{eff}^2}{2V_{DD}^2}$$

F. H. Raab, "Maximum efficiency and output of class-F power amplifiers," *IEEE Trans. Microwave Theory Tech.*, vol. 49, no. 6, pp. 1162 - 1166, June 2001.

# Class-A and AB PAs

## Transmission-lines and Lumped Elements



Class-A or AB  $\eta = 50$  to  $60\%$

$$Z_{VD} = R_L$$


$$\gamma_V = 1$$

$$\gamma_I = 1$$

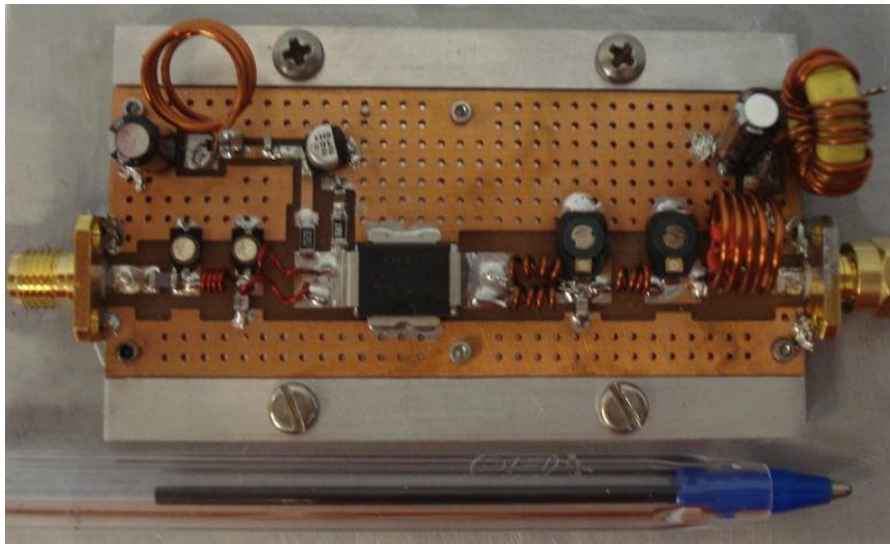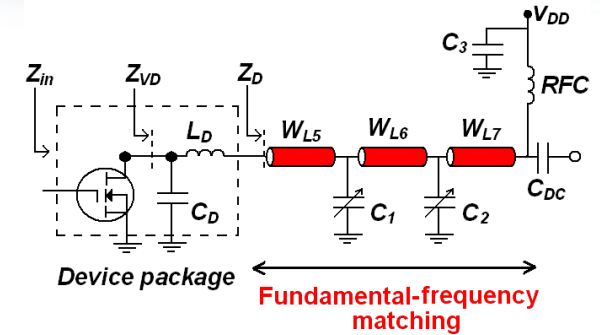It doesn't require harmonic component neither in drain voltage nor in drain current waveforms



ST LDMOS FET PD57070

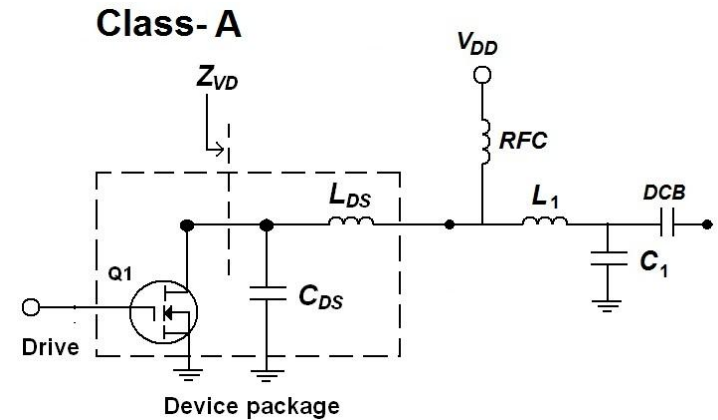

Efficiency: 35% in Class-A Output power: 70 Watts Frequency band: 290-390 MHz



# Class-B PA implementation

## Transmission-lines and Lumped Elements



Class-B<sub>2</sub>  $\eta = 70.71\%$

$Z_{VD} = R_L$  at  $f_0$   
 $= 0$  at  $2f_0$


$$\gamma_V = 1$$

$$\gamma_I = 1.4142$$

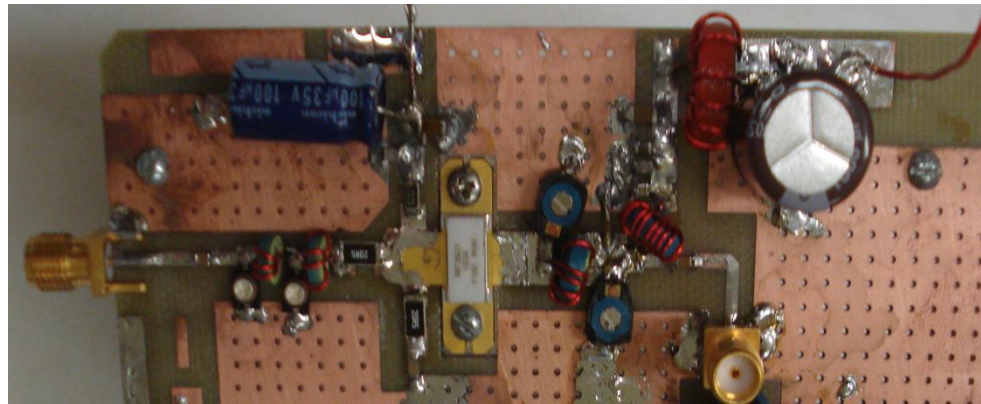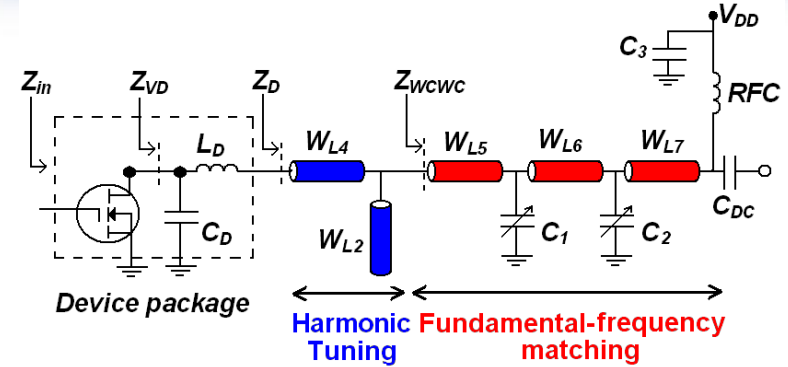It requires harmonic component in drain current waveforms




GaN FET RF3931

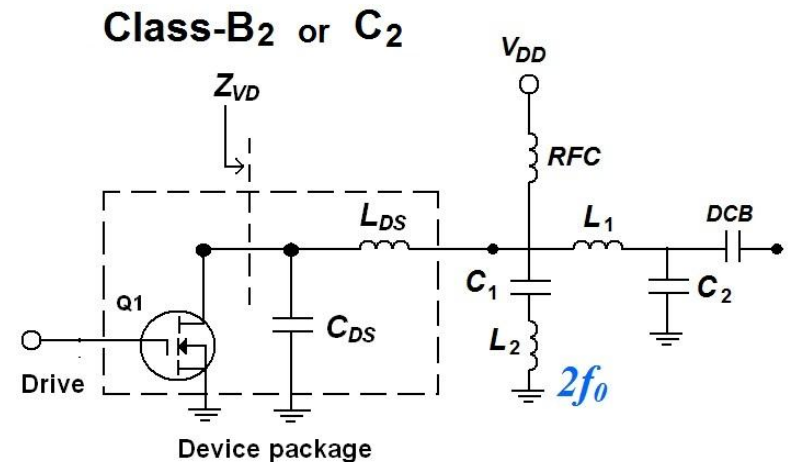

Efficiency: 65%; Output power: 5 Watts; Frequency 144-MHz

# Class-C and D
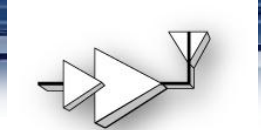
## Transmission-lines and Lumped Elements



Class-C can be regarded as a reduce conduction angle class-B with a large number of harmonic currents added at VD.


$$Z_{VD} = R_L \text{ at } f_0$$

$$= 0 \text{ at } 2f_0$$

$$\eta = 78.5 \%$$

$$\gamma_V = 1$$
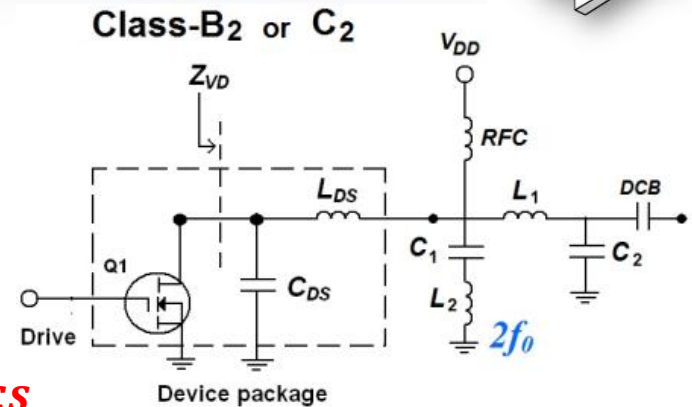
$$\gamma_I = 1.571 \text{ all harmonics}$$



Class D is a push-pull class-F PA


-the two active devices provide each other with paths for the even harmonics.

Therefore, class-D PA is related to class-F<sub>2,3</sub> as explain later.

$$\eta = 81.65 \%$$


$$\gamma_V = 1.1547$$

$$\gamma_I = 1.4142$$

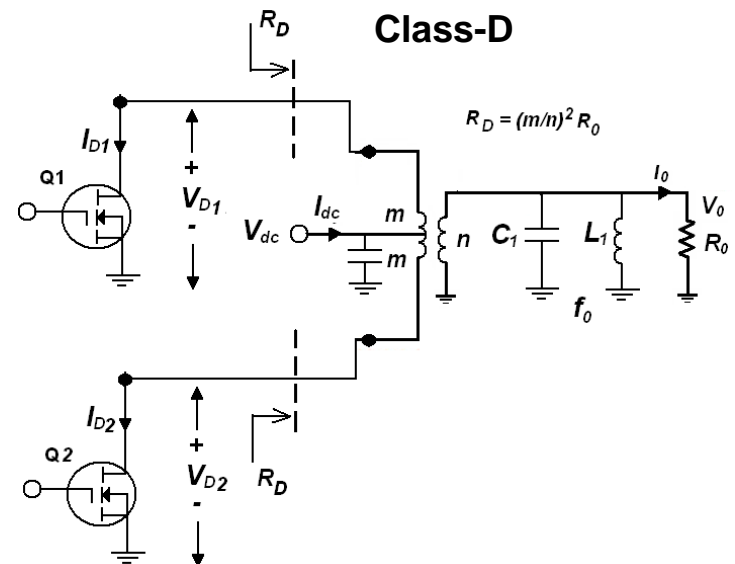

# Class-E

## True-Transient Suboptimum Operation

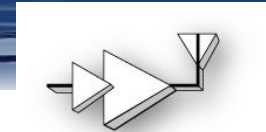


Class-E<sub>10</sub>  $\eta = 100\%$


$$Z_{VD} = R_L + jX_L \text{ at } f_0$$

$$= -j5.4466 \cdot R_0/n \text{ at } nf_0$$

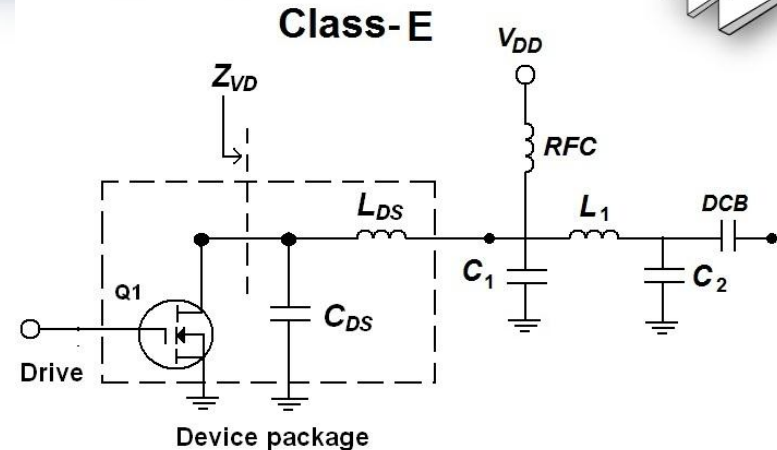
Harmonic impedances are not just short circuits.



Ideal true-transient waveforms 

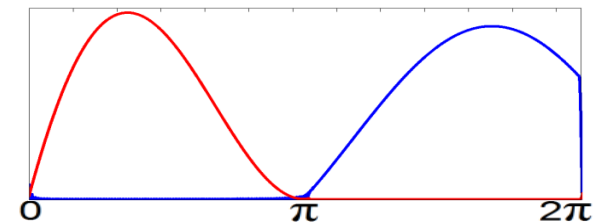


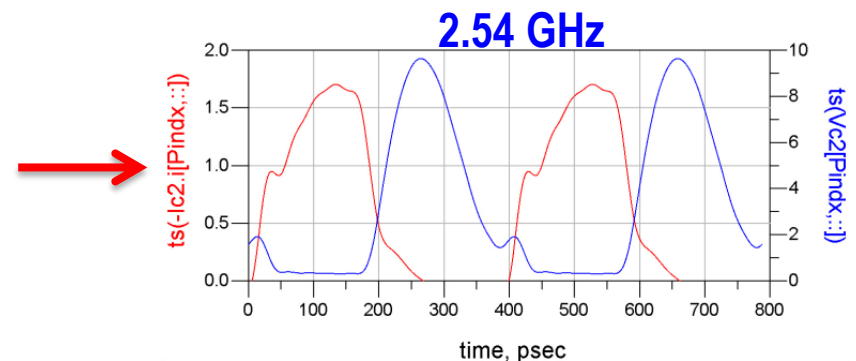Generally mistuned at high-frequencies  
It is a good approximation if we have access to the intrinsic drain



# Class-E Amplifier Reactances

## Impedances for ideal Class-E

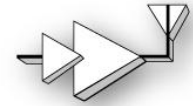

### Specific Drain Impedances $Z_{VD}$

Freq.	Ideal Class-E $R_0=10\text{-Ohms}$
$f_0$	15.26+j11.064
$2f_0$	-j27.23
$3f_0$	-j18.15
$4f_0$	-j13.61
$5f_0$	-j10.89
$6f_0$	-j9.03
$7f_0$	-j7.78
$8f_0$	-j6.77
$9f_0$	-j6.05
$10f_0$	-j5.42

$V_{DD} = 15\text{ V}$   
 $P_{out} = 11.5\text{-W}$

$Z_{VD} = (1.526+j1.106) \cdot R_0$

$B_S = 0.1836/R_0$   
 $X_S = 1.15 \cdot R_0$

$X_n = -j5.4466 \cdot R_0/n$

# Class-E<sub>2</sub>

## Second harmonic Approximation to Class-E Operation

Class-E<sub>2</sub>  $\eta = 70.71\%$


$$Z_{VD} = R_L + jX_L \text{ at } f_0$$

$$= -jX_2 \text{ at } 2f_0$$



$$\gamma_V = 1.4142$$

$$\gamma_I = 1.4142$$

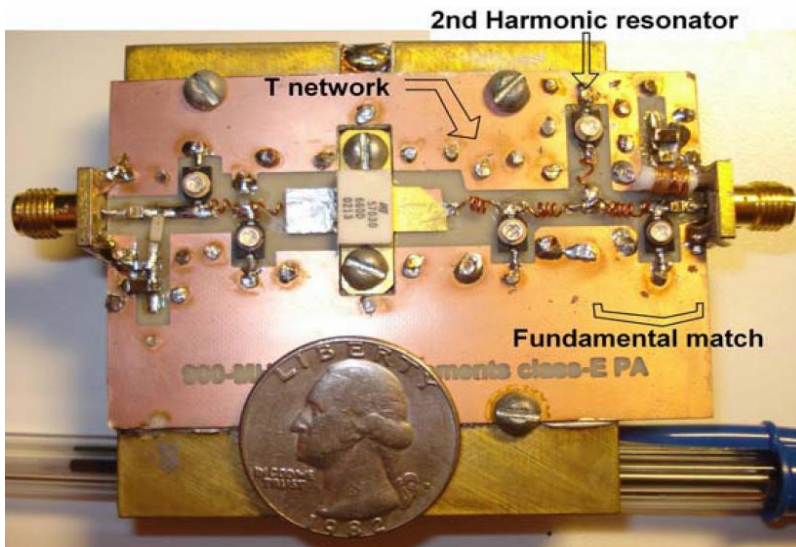The 2<sup>nd</sup> harmonic in drain current waveform requires A GIVEN REACTANCE (not just a short)




ST LDMOS FET SD57030

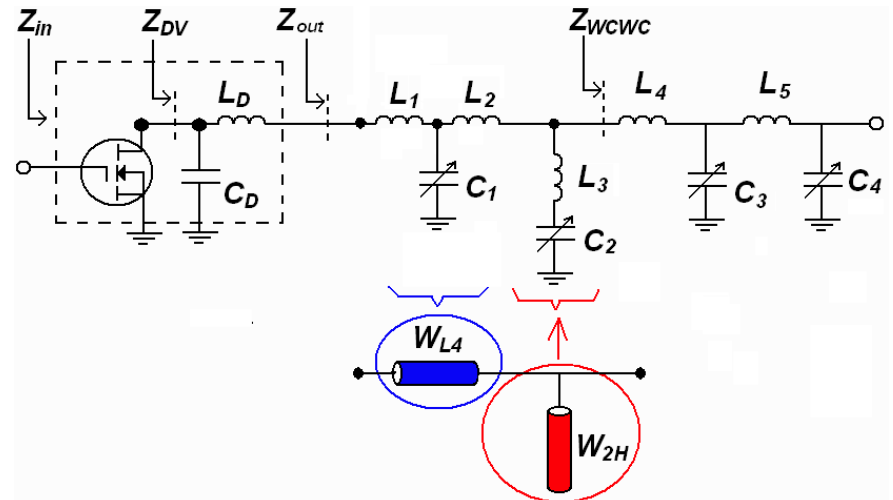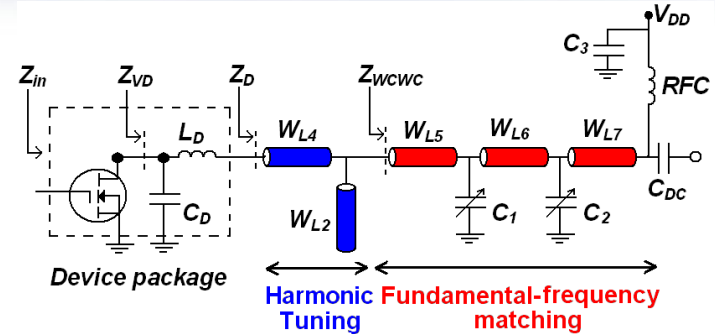

Efficiency: 67%; Output power: 10 Watts; Frequency 900-MHz

# Class-E<sub>2</sub>
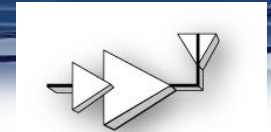
## Second harmonic Approximation to Class-E Operation



### Fundamental and Second harmonic Impedances

$$V_{DD} = 15 \text{ V}$$

$$P_{out} = 11.5 \text{ W}$$


Freq.	Class-E <sub>2</sub>
$f_0$	$8.86 + j8.86$
$2f_0$	$-j12.28$
$3f_0$	NA
$4f_0$	NA
$5f_0$	NA
$6f_0$	NA
$7f_0$	NA
$8f_0$	NA
$9f_0$	NA
$10f_0$	NA

←  $Z_{VD} = R_1 + jR_1$

←  $X_2 = -j1.414R_1$

Second harmonic voltage and current in phase quadrature (no power dissipation)


Class-E<sub>2</sub> drain waveforms

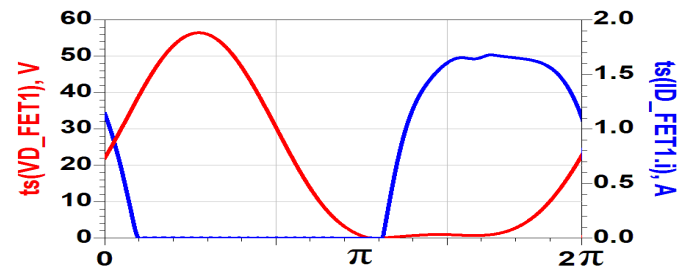





# Class-E Multi-harmonic Approximation

## Impedances for Class-E<sub>10</sub>

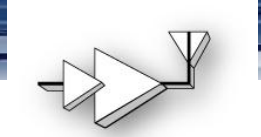


Class-E<sub>10</sub>  $\eta = 85\%$   
 $Z_{VD} = R_L + jX_L$  at  $f_0$   
 $= -j5.4466 \cdot R_0/n$  at  $nf_0$

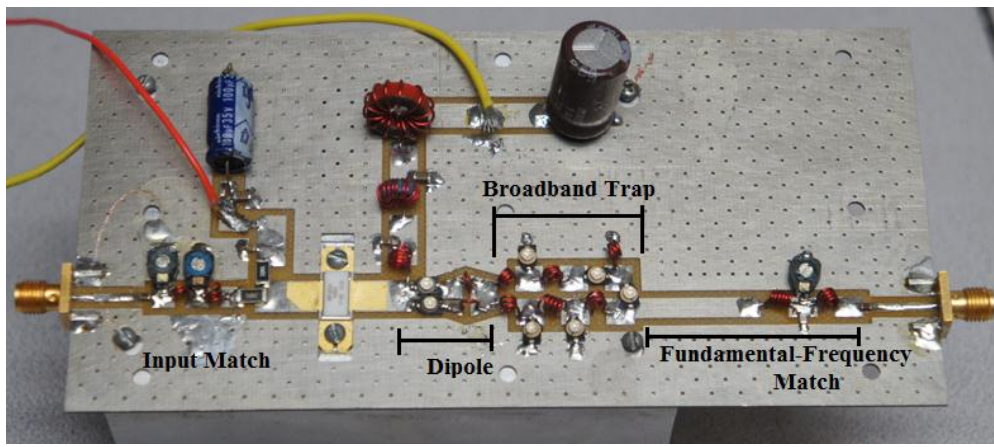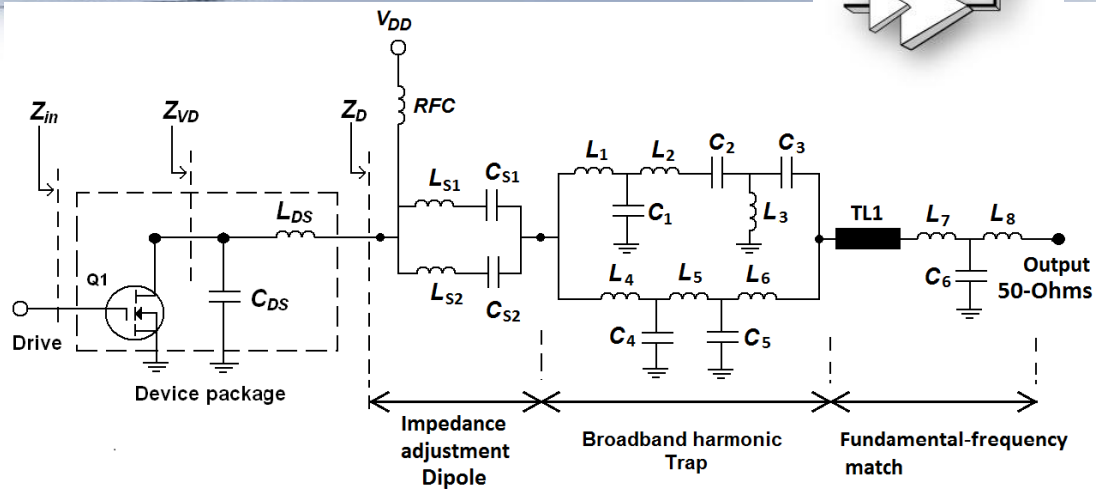It requires harmonic drain currents and voltages with specific reactance values




GaN FET RF3931

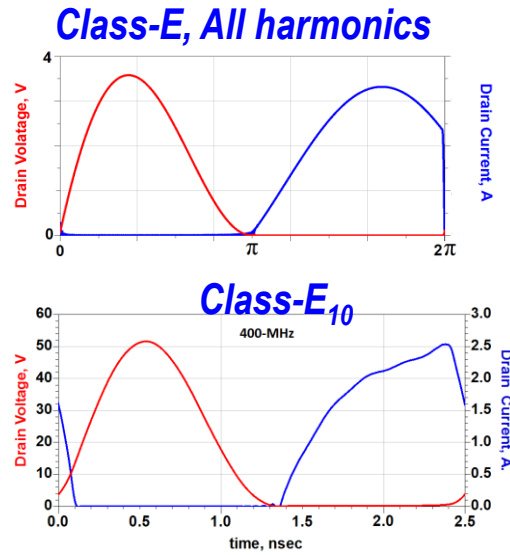

Efficiency: 85%; Output power: 10 Watts; Frequency 400-MHz

# Class-E Multi-harmonic Approximation

## Impedances for Class-E<sub>10</sub>

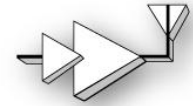

Comparison between ideal class-E and class-E<sub>10</sub>

$V_{DD} = 15\text{ V}$   
 $P_{out} = 11.5\text{-W}$

Freq.	Ideal Class-E	Class-E <sub>10</sub>	Ratio E <sub>10</sub> /E
$f_0$	15.26+j11.064	<b>15.26+j11.064</b>	1
$2f_0$	-j27.23	<b>-j27.23</b>	1
$3f_0$	-j18.155	<b>-j9.881</b>	0.544
$4f_0$	-j13.616	<b>-j5.144</b>	0.377
$5f_0$	-j10.893	<b>-j3.952</b>	0.363
$6f_0$	-j9.038	<b>-j3.226</b>	0.357
$7f_0$	-j7.781	<b>-j2.684</b>	0.345
$8f_0$	-j6.778	<b>-j2.269</b>	0.335
$9f_0$	-j6.052	<b>-j1.892</b>	0.312
$10f_0$	-j5.420	<b>-j1.378</b>	0.254



# Class-F<sub>2,3</sub> Power Amplifier

Second and third harmonic

Class-F<sub>2,3</sub>  $\eta = 81.65\%$

$$Z_{VD} = R_L \text{ at } f_0$$



$$= 0 \text{ at } 2f_0$$

$$= \infty \text{ at } 3f_0$$


$$\gamma_V = 1.1547$$

$$\gamma_I = 1.4142$$

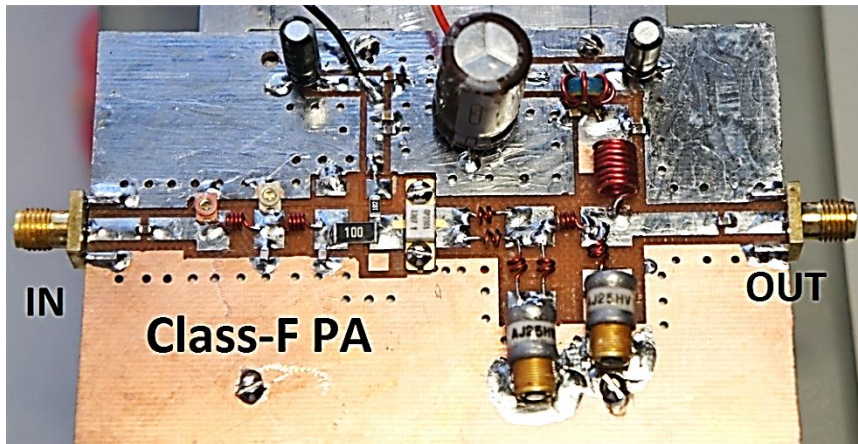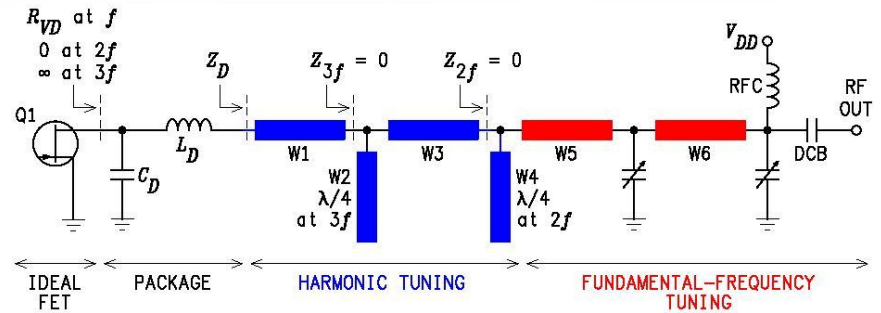It requires harmonic voltage and current at drain waveforms.



GaN FET GP2001 PolyFET

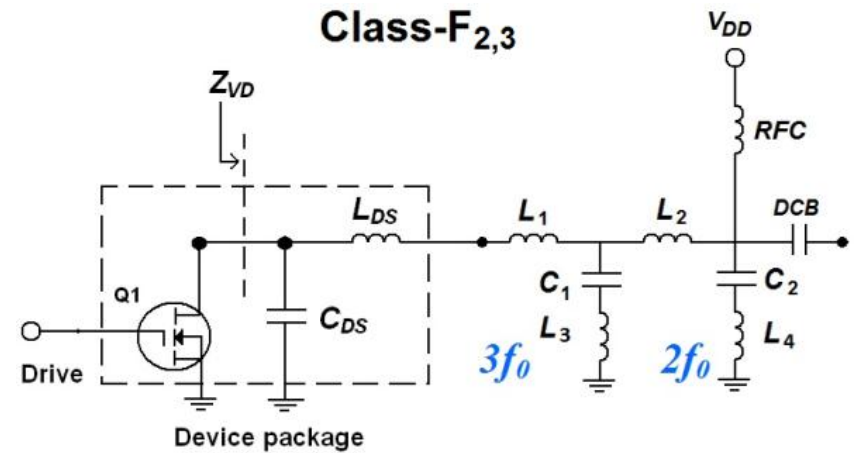

Efficiency: 81%; Output power: 17 Watts; Frequency 300-MHz

# Inverse Class-F<sub>2,3</sub> Power Amplifier

Second and third harmonic



Class-F<sub>2,3</sub>  $\eta = 81.65\%$

$Z_{VD} = R_L$  at  $f_0$   
 $= \infty$  at  $2f_0$   
 $= 0$  at  $3f_0$


$\gamma_V = 1.1547$

$\gamma_I = 1.4142$

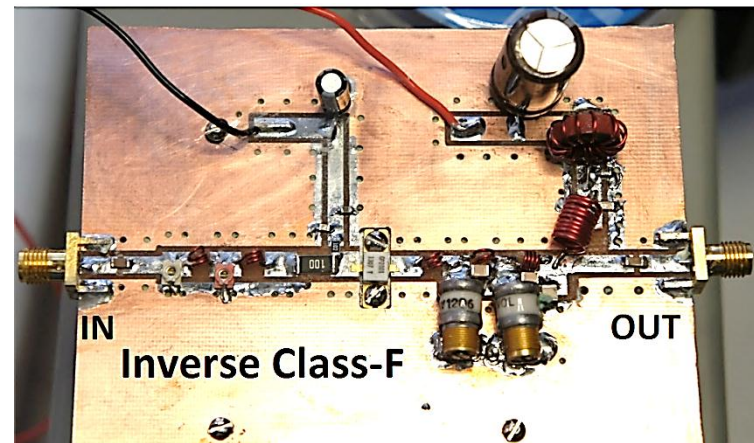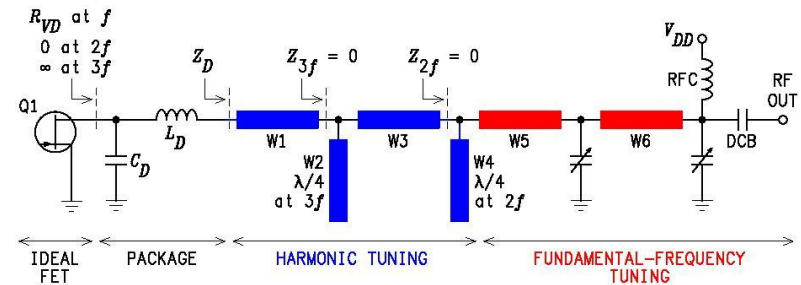It requires harmonic voltage and current at drain waveforms.




GaN FET GP2001 PolyFET

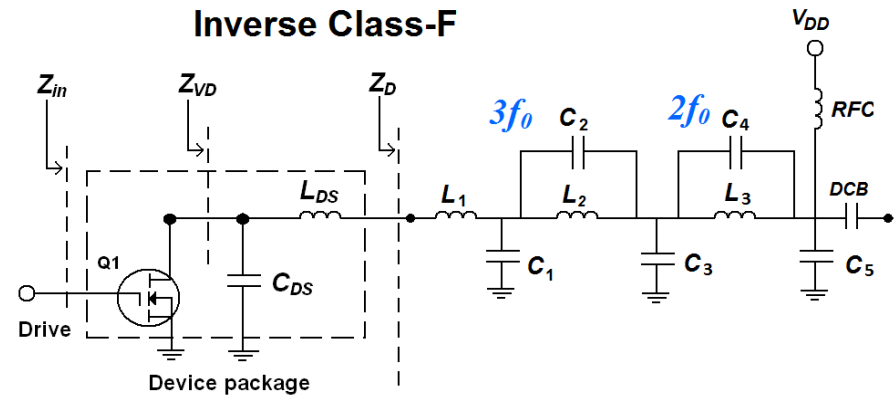


Efficiency: 79%; Output power: 17 Watts; Frequency 300-MHz

# Impedances for PA classes

*Impedances at intrinsic drain*

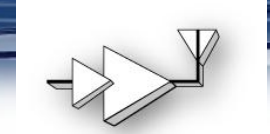


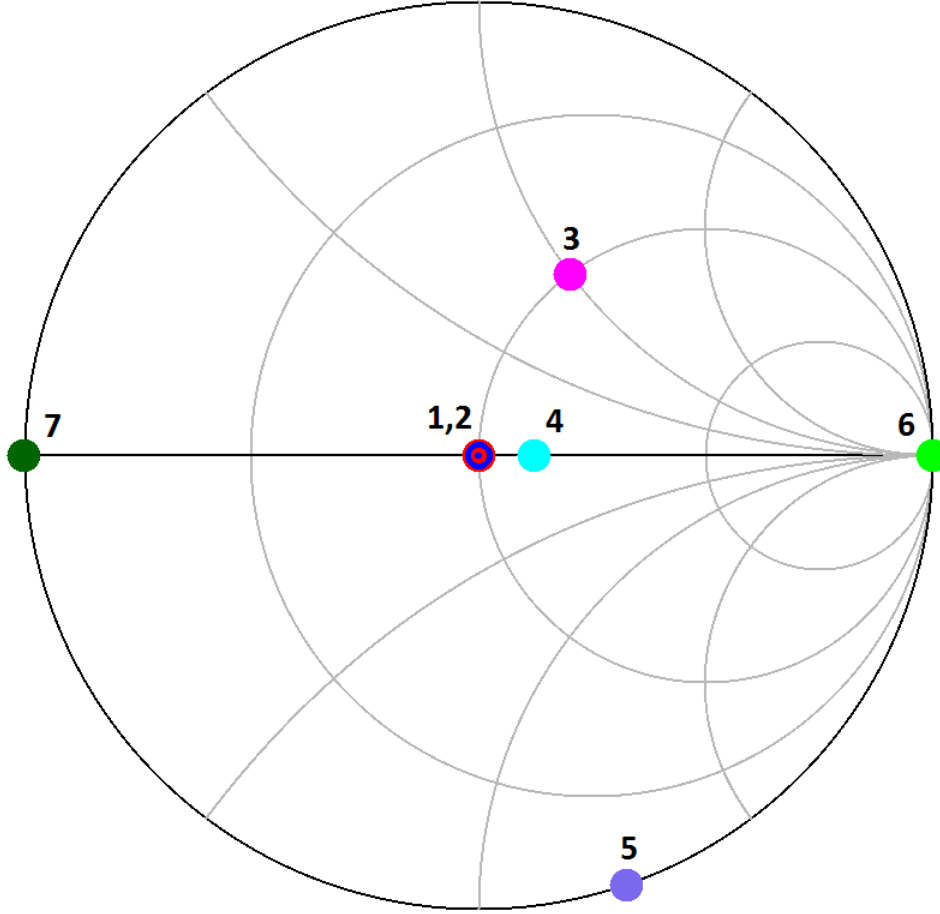Class\_AB\_B\_C\_F\_2fo 7  
Class\_F23\_3fo 6  
Class\_E2fo 5  
Class\_F23 4  
Class\_E2 3  
Class\_B 2  
Class\_A 1




# Continuous Class-E<sub>2</sub> and F<sub>2,3</sub>

## Impedance locus

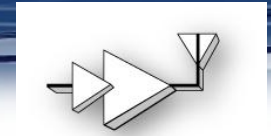

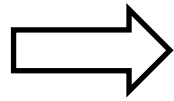
Do you remember the waveform factor for class-B<sub>2</sub> and class-E<sub>2</sub> are the same?



$$\gamma_I = 1.4142$$


There is a transition from class-E<sub>2</sub> to class-B<sub>2</sub> PAs.

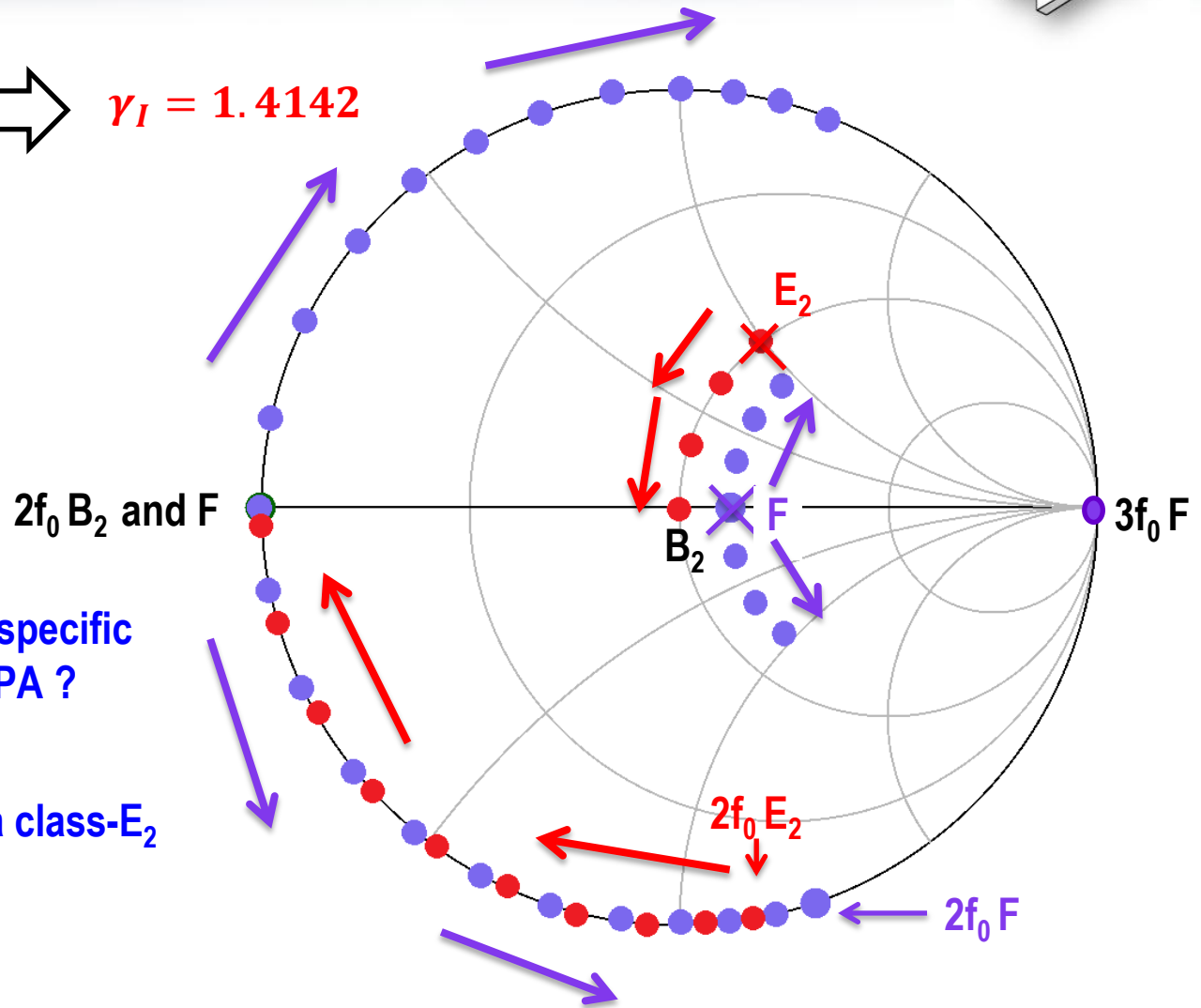- Does class-J look like an specific solution case of class-E<sub>2</sub> PA ?
- A harmonic load-pull for a class-E<sub>2</sub> PA will reveal the true.



# Power Amplifiers for RF Transmitters

*Enhancing efficiency at back-off*

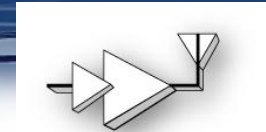

$$Efficiency = \frac{P_o}{P_{DC}}$$

Maximize  $P_o$

Minimize or keep same  $P_{DC}$

**ET, EER, DC-DC**



$$P_o = \frac{(\gamma_V \cdot V_{eff})^2}{2R_L}$$




**Doherty and Outphasing**




# Using PAs in Outphasing and Doherty



## Load modulation for PAs

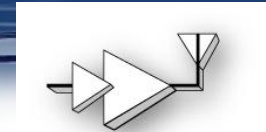

### H. Chireix

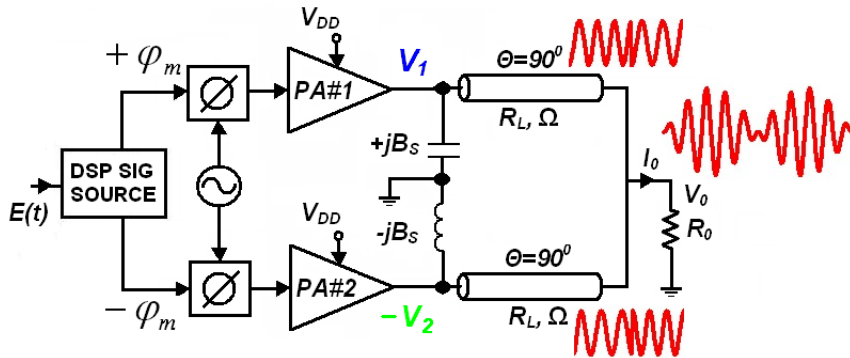


### W. Doherty

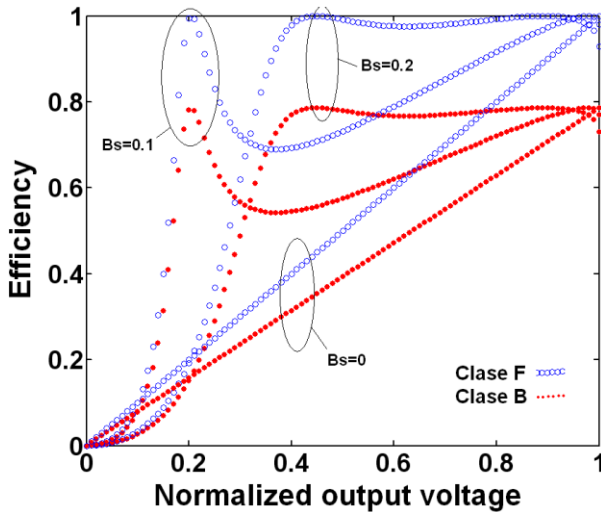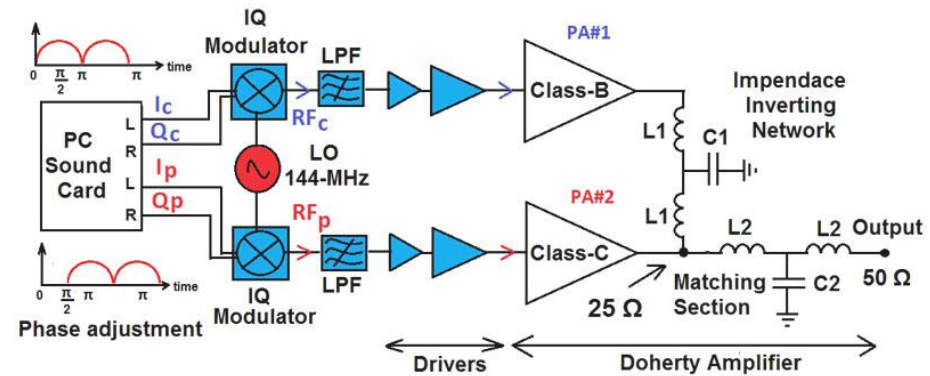

Class-B PAs


and/or

Class-F PAs

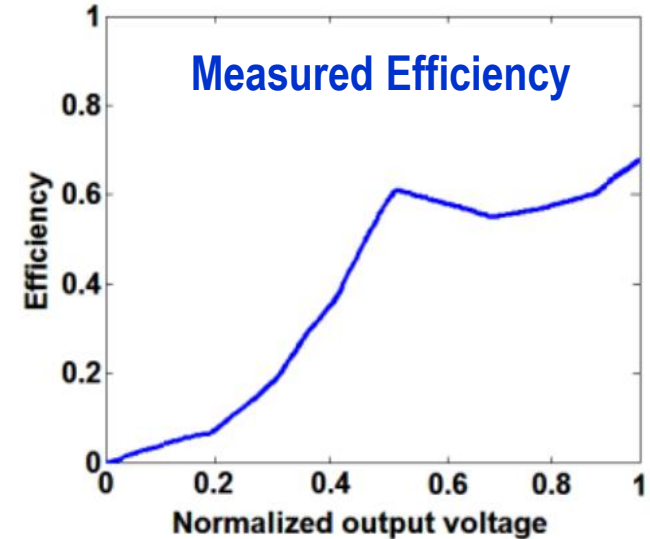


# Load Modulation for PA classes
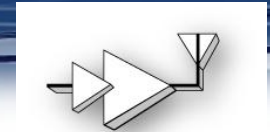
## Impedance locus for a voltage source PA





Why a real amplifier does not work as expected for Outphasing or Doherty transmitters?

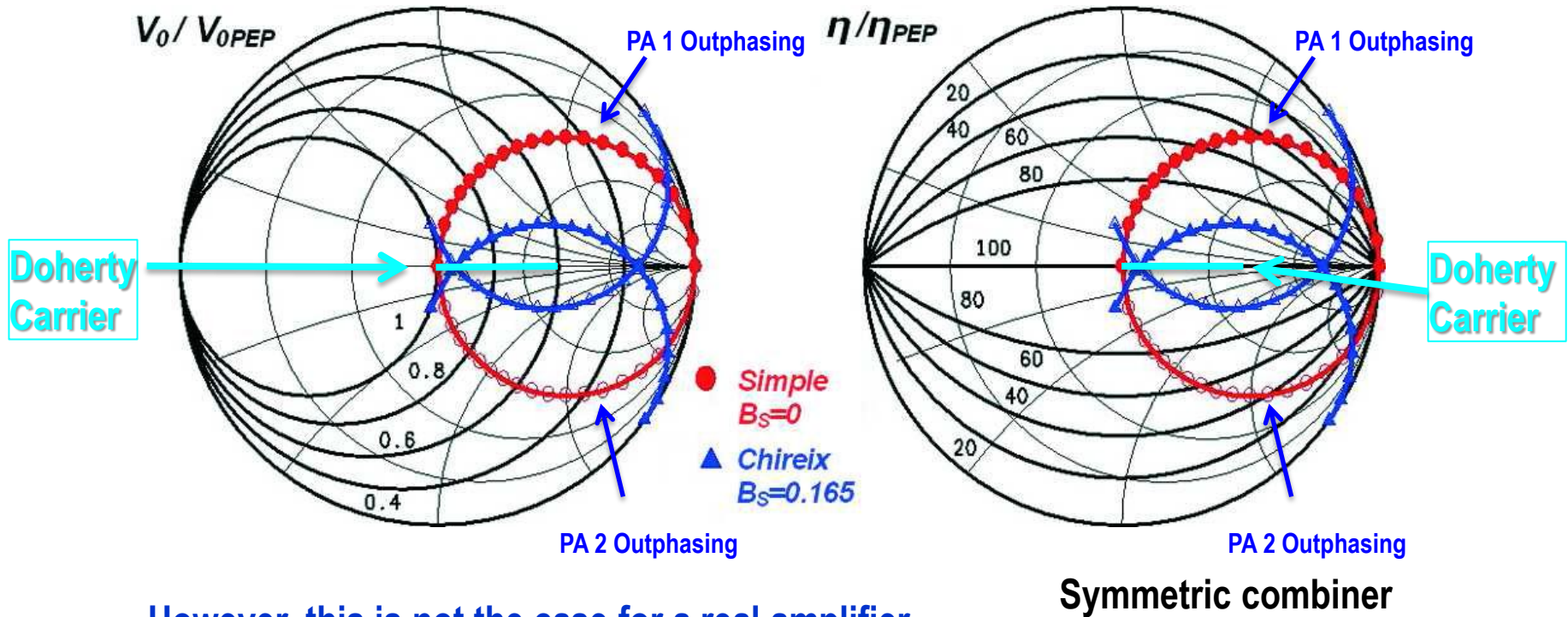Don't use a real PA assuming ideal load-pull contours




However, this is not the case for a real amplifier...
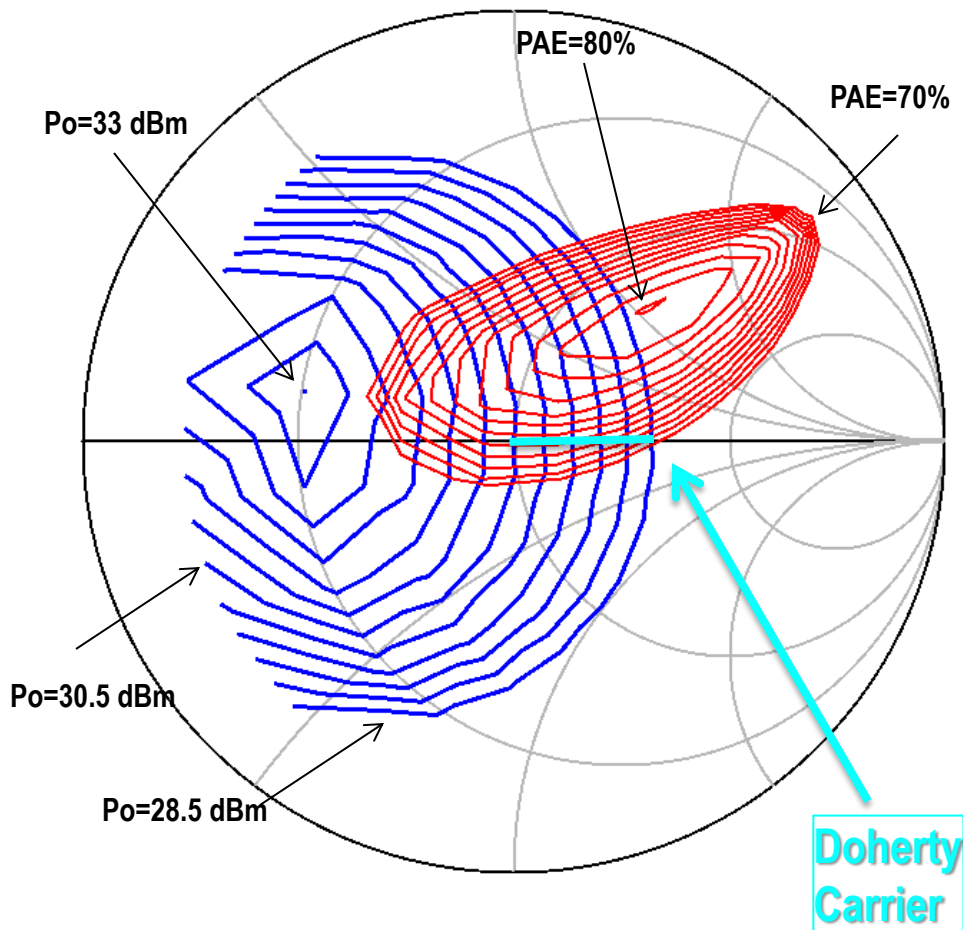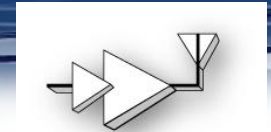
# Load Modulation for real PAs and Asymmetric Combining




Chireix Asymmetric

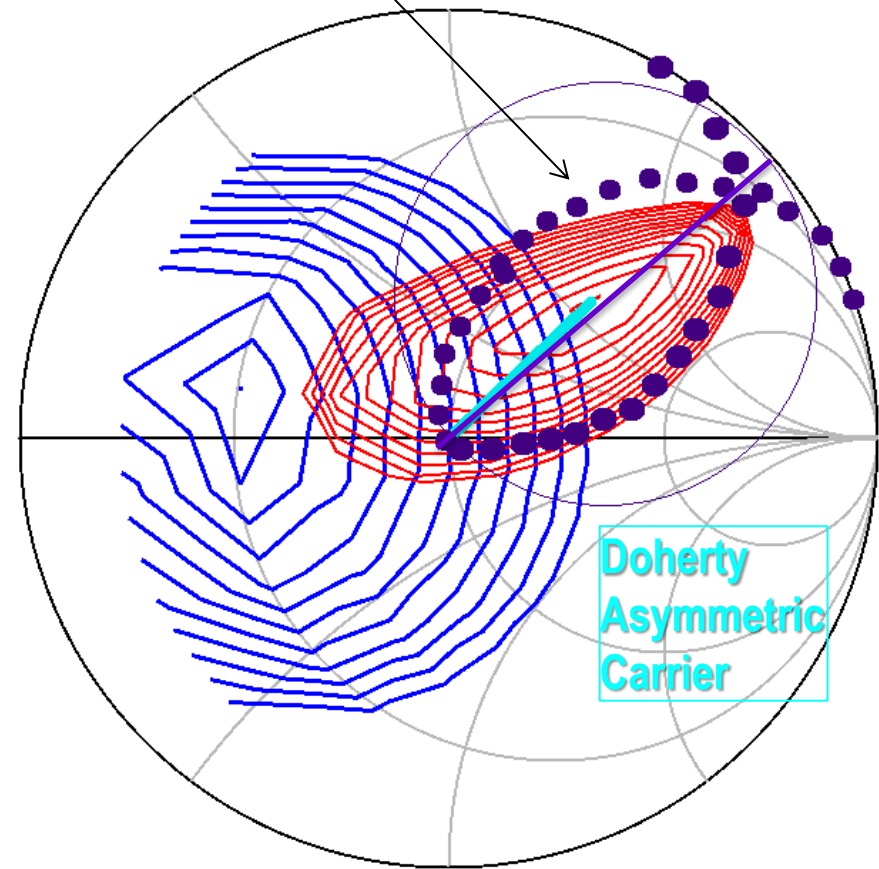

Asymmetric combiner



# Summary -

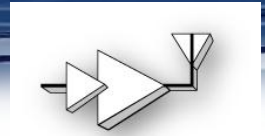

- The power amplifier efficiency depends upon the number of controlled harmonics.
- The harmonic impedances define the amplifier's output power capabilities and waveform shapes.
- Lumped-element output networks can serve for a wide frequency range.
- For a load modulated amplifier (i.e Doherty or Outphasing) take a look at the amplifiers load-pull contours, since they may need asymmetric combining.
- Not all real amplifiers can operate in either classic Doherty or Outphasing. However, DSP assisted PAs systems could overcome practical limitations by compensating phase and amplitude unbalance as well as other parameters such as linearity through pre-distortion.
- The transition between PA classes is one of the most common confusion in a real amplifier when it is tuned in the measurement bench.



**Power Amplifier Classes Based upon Harmonic Approximation and Lumped-element Loading Networks**

**Thank you all**

**Questions?**